



EDU ***ENGINEERING***

PIONEER OF ENGINEERING NOTES

CONNECT WITH US




WEBSITE: www.eduengineering.in



TELEGRAM: [@eduengineering](https://t.me/eduengineering)

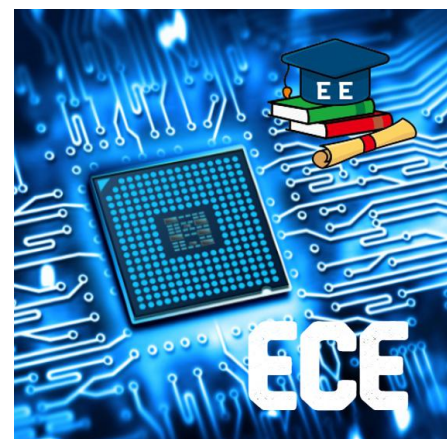- Best website for **Anna University Affiliated College** Students
- Regular Updates for all Semesters
- All **Department Notes** AVAILABLE
- All **Lab Manuals** AVAILABLE
- **Handwritten** Notes AVAILABLE
- **Printed** Notes AVAILABLE
- **Past Year** Question Papers AVAILABLE
- Subject wise **Question Banks** AVAILABLE
- Important Questions for Semesters AVAILABLE
- Various Author Books AVAILABLE



Definitions:-

Electrical circuit:- It is a closed path of wires and electrical components which allows a current through it.

Circuit Diagram:- It is a graphical representation of an electric circuit, It shows the components and interconnections of the circuit using symbols.

Voltage (V) voltage is the difference in electric Potential between two points, that pushes charged electrons (current) through a conducting loop.

Unit is volts (V)

Voltage is represented by the letter 'V' or 'E' current (I)

Current is the rate of flow of electric

charge

Unit is amperes (A)

Current is represented by the letter 'I'.

Resistance:- (R)

Resistance is a measure of the opposition to the current flow in an electrical circuit.

It is represented by the letter 'R'

Unit of Resistance = Ω (ohms)

Resistor:-

Components that offer Resistance.

Conductance: (G)

Conductance is the reciprocal of resistance

$$G = 1/R$$

Unit of conductance is Ω (mho)

Charge:-

Amount of energy or electrons that pass from one body to another.

Colomb's Law: - Attraction or repulsion between two electric charges.

TELEGRAM: @studengsintering

TECHNOLOGY

Symbols


Resistance/Resistor:-



DC voltage Source:-



DC Current Source:-

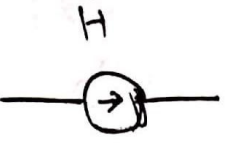

Ammeter:-

- * Ammeter is used to measure current
- * It should be connected in series



Voltmeter:-

- * Voltmeter is used to measure voltage.

or potential difference between two points in a circuit.



Connection cable:-




Variable Resistor:-



Value of the resistor is variable in such kind of resistors.

Basic components of Electric circuits:-

- * Branch,
- * Nodes.
- * Loops.

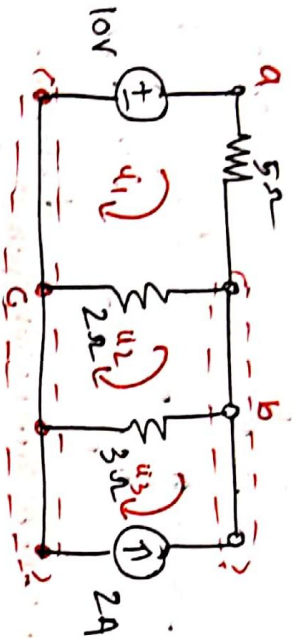

Branches:-

A branch represents a single element such as a voltage source or a resistor.

In the above circuit, 10V-voltage source, 2A-current source, 5Ω, 2Ω, & 3Ω Resistors are the branches.

Node:

A Node is a Point of connection between two or more branches.

Point a, b, c are nodes of the circuit.

If a short circuit (a connecting wires)

connects two nodes, the two nodes constitute a single node. (Even though 3 points are there near point 3 they are considered as single node)

Loop

A loop is a closed path formed by starting at a node, passing through the a set of nodes and returning to the starting node.

abca → forms first loop.

bcb → forms second loop / third loop.

eg.



abca → 1st loop

bcb → 2nd loop

dced → 3rd loop

i_1, i_2, i_3 → are called as loop currents.

Series & Parallel Circuits:-



Resistor R_1 & R_2 are said to be in series because the same current 'I' flows in both the resistors.

$$R_{eq} = R_1 + R_2$$

Total Resistance or equivalent Resistance is

the sum of the two resistors or 'n' resistors.

$$R_{eq} = R_1 + R_2 + \dots + R_n \quad \text{for 'n' resistors connected in series.}$$


eg.



Same 5A is flowing in both 10Ω & 20Ω. So they are connected in series.

$$R_{eq} = 10 + 20 = 30\Omega$$

Parallel Circuit / Shunt Circuit.

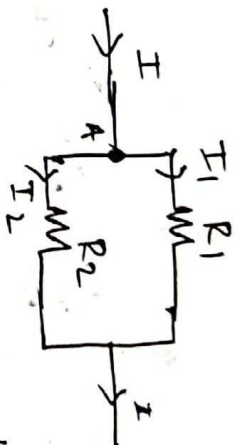


Resistors R_1 & R_2 are said to be connected in parallel, because different currents (I_1 in R_1 & (I_2 in R_2) are flowing.

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$


or

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

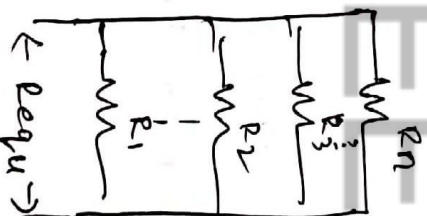

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$

eg:-

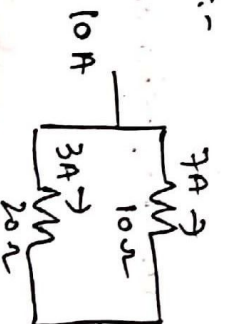

In this circuit total current enters is 10A, it is split 4A enters 10Ω & 3A enters 20Ω, so, 10Ω & 20Ω are

in parallel

Ohm's law:-

Ohm's law states that at constant temperature the voltage across a conductor is directly proportional to the current flowing through it.

$$V \propto I$$

$$V = IR$$

$$V = IR \text{ in volts}$$

$$I = V/R \text{ in amp}$$

$R \Rightarrow$ Resistance.

$$R = V/I \text{ in ohms.}$$

Problem:-


- ① An electric iron draws 2A at 10V, find its resistance

From Ohm's law

$$R = \frac{V}{I} = \frac{10}{2} = 5\Omega$$

$$R = 5\Omega$$

②

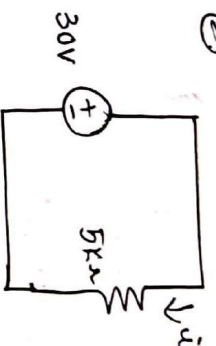

In the circuit shown, calculate the current 'i', conductance 'G' and Power 'P'.

Solution:-

Current:- $i = V/R$

$$= \frac{30}{5 \times 10^3} \rightarrow (5k = 5 \times 10^3 \Omega \text{ or } 5000 \Omega)$$

$$i = 6 \text{ mA} \quad (6 \text{ milliamps})$$

Conductance G

$$G = \frac{1}{R} = \frac{1}{5 \times 10^3} = 0.2 \text{ mS or } 0.2 \text{ m}\Omega$$

0.2 mS

$$G = 0.2 \text{ m}\Omega$$

(where S is Siemens)
(m $\rightarrow$ represent milli;
 10^{-3})

Power (P)

$$\text{Power } P = V \times I = 30 \times (6 \times 10^{-3})$$

$$P = 180 \text{ mW}$$


Kirchoff's Law:-

- * Kirchoff's current law (KCL)
- * Kirchoff's voltage law (KVL)

Kirchoff's current law (KCL)

EC 3251 Circuit Analysis

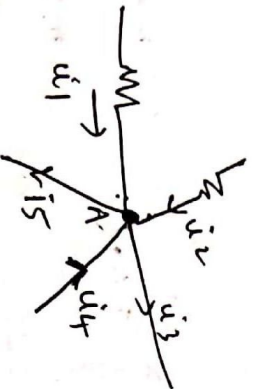Kirchoff's current law states that the sum of the currents entering a node is equal to the sum of the current leaving the node (or) in other words algebraic sum of the currents at node is zero.



In the figure above 'A' is the node, currents entering the node are i_1, i_2, i_3 (see the arrow mark for direction) and currents leaving the node are i_4 & i_5 .

So according to KCL


$$i_1 + i_2 + i_4 = i_3 + i_5$$

or

$$i_1 + i_2 + i_4 - i_3 - i_5 = 0$$

Problem:-

Unit I DC Circuit A

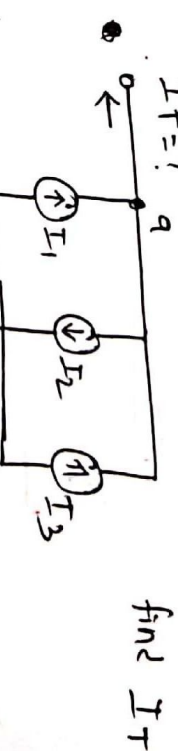find I_T SolutionAt node 'a' I_1 & I_3 are entering. I_2 & I_T are leavingSo according to KCL $I_T + I_2 = I_1 + I_3$


$$I_T = I_1 + I_3 - I_2$$

Kirchoff's Voltage Law: (KVL)

Kirchoff's voltage law states that the algebraic sum of all voltages around a closed path or loop is zero.

or in other words. In a closed circuit.

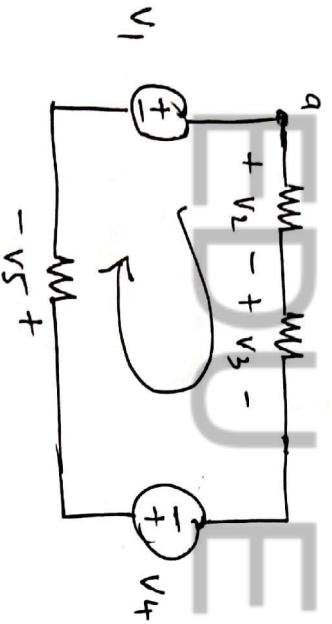Sum of the Potential raise = Sum of the Potential drops.



Let's start from point 'a' & traverse the loop.

$$+V_2 + V_3 - V_4 + V_5 - V_1 = 0$$

$$V_1 + V_4 = V_2 + V_3 + V_5$$

V_1 & V_4 = Potential raise, V_2, V_3 & V_5 = Potential drops.


Concept to remember:-

If current I_1 flows in a resistor R_1 , then a voltage drop V_1 occurs at the resistor R_1 with the polarity shown.



Polarity of the voltage depends on the direction of the current entry. increased

Problems:

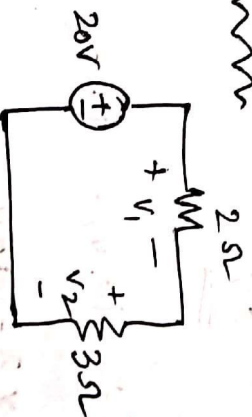

find the voltages V_1 & V_2 for the circuit shown.

Solution:-

To find V_1 & V_2 , we need to find the current flowing through the resistors.

* To find the total current we need to find the equivalent resistances of this circuit.

* Resistance $R_{2\Omega}$ & 3Ω are connected

in series (since the same current flows)

$$R_{eq} = 5\Omega \quad (2+3)$$

Total current $i =$

$$V/R = \frac{20}{5} = \underline{\underline{4A}}$$

Voltage drop across 2Ω i.e. $V_1 = I \times R_1$

$$4 \times 2 = \underline{\underline{8V}}$$

$$\boxed{V_1 = 8V}$$

Voltage drop across 3Ω i.e. $V_2 = I \times R_2$

$$4 \times 3 = \underline{\underline{12V}}$$

Verification

$$\boxed{V_2 = 12V}$$

According to KVL voltage rise = voltage drops

$$20V = 8V + 12V$$


Voltage

rise

voltage drops

EDU ENGINEERING

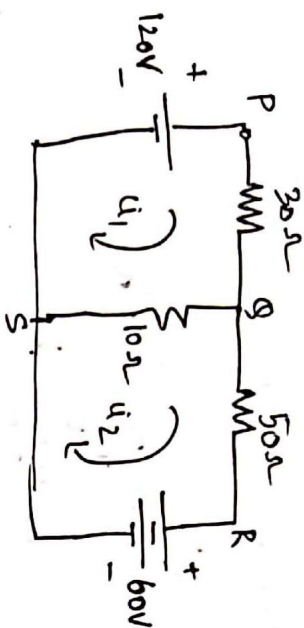1. Solve the mesh and branch currents for the circuit shown.



Solution:-

Apply KVL at loop 1 (P Q S P)

$$30i_1 + 10(i_1 - i_2) = 120$$

$$40i_1 - 10i_2 = 120 \quad \text{--- (1)}$$

Apply KVL at loop 2 (Q R S Q)

$$50i_2 + 10(i_2 - i_1) = -60$$

$$-10i_1 + 60i_2 = -60 \quad \text{--- (2)}$$

By using Cramer's rule find Δ

$$\Delta = \begin{bmatrix} 40 & -10 \\ -10 & 60 \end{bmatrix} = (60 \times 40) - (-10 \times -10)$$

$$\Delta = 2300$$

$$\Delta_1 = \begin{bmatrix} 120 & -10 \\ -60 & 60 \end{bmatrix} = (120 \times 60) - (-10 \times -60)$$

$$= 7200 - 600$$

$$\Delta_1 = 6600$$

$$\Delta_2 = \begin{bmatrix} 40 & 120 \\ -10 & -60 \end{bmatrix} = (40 \times -60) - (-10 \times 120)$$


$$= -2400 + 1200$$

$$\Delta_2 = -1200$$

$$i_1 = \frac{\Delta_1}{\Delta} = \frac{6600}{2300} = \underline{\underline{2.86 \text{ A}}}$$

$$i_2 = \frac{\Delta_2}{\Delta} = \frac{-1200}{2300} = \underline{\underline{-0.521 \text{ A}}}$$

i_1 & i_2 are loop currents.

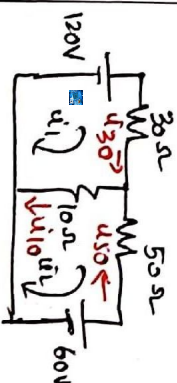

i_{30} , i_{50} & i_{10} are called branch currents.
(Simply the current at the branches).

$$\begin{aligned} i_{30} = i_1 &= 2.86 \text{ A} \\ i_{50} = i_1 - i_2 &= 0.521 \text{ A} \\ i_{10} = i_{30} + i_{50} &= 3.381 \text{ A} \end{aligned}$$

Note:-


i_{50} is opposite to i_2 so $i_{50} = -i_2$.

Current i_{30} & i_{50} combine & flow in

10 Ω resistor so $i_{10} = i_{30} + i_{50}$.

i_1 & i_{30} are same so $i_1 = i_{30}$.
(Refer the circuit).

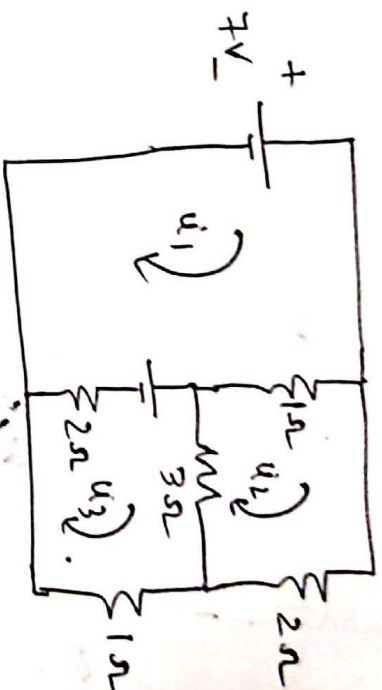2) Use the mesh analysis to determine the three mesh currents in the circuit shown.



Three loops are there in this circuit. loop 1, 2, 3.
apply KVL in loop 1:-

$$1(i_1 - i_2) + 2(i_1 - i_3) = 7 - 6$$

$$3i_1 - i_2 - 2i_3 = 1 \quad \text{--- (1)}$$

Loop 2

$$1(i_2 - i_1) + 2(i_2) + 3(i_2 - i_3) = 0$$

$$-i_1 + 6i_2 - 3i_3 = 0 \quad \text{--- (2)}$$

Loop 3

$$3(i_3 - i_2) + 1i_3 + 2(i_3 - i_1) = 6$$

Matrix representation:-

$$\begin{bmatrix} 3 & -1 & 2 \\ -1 & 6 & -3 \\ -2 & -3 & 6 \end{bmatrix} \begin{bmatrix} u_1 \\ u_2 \\ u_3 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \\ 6 \end{bmatrix}$$

$$A = \begin{bmatrix} 3 & -1 & 2 \\ -1 & 6 & -3 \\ -2 & -3 & 6 \end{bmatrix}$$

$$= 3(36-9) + 1(-6-6) - 2(3+12) \\ = 81 - 12 - 30$$

$$\Delta = 39$$

$$\Delta_1 = \begin{vmatrix} 1 & -1 & -2 \\ 0 & 6 & -3 \\ 6 & -3 & 6 \end{vmatrix}$$

$$\Delta_2 = \begin{vmatrix} 3 & 1 & -2 \\ -1 & 0 & -3 \\ -2 & 6 & 6 \end{vmatrix}$$

$$\Delta_3 = \begin{vmatrix} 3 & -1 & 1 \\ -1 & 6 & 0 \\ -2 & -3 & 6 \end{vmatrix}$$

$$\Delta_1 = 117$$

$$\Delta_2 = 78$$

$$\Delta_3 = 117$$

$$u_1 = \frac{\Delta_1}{\Delta} = \frac{117}{39} = 3A$$

$$u_2 = \frac{\Delta_2}{\Delta} = \frac{78}{39} = 2A$$


$$u_3 = \frac{\Delta_3}{\Delta} = \frac{117}{39} = 3A$$

$$u_1 = 3A$$

$$u_2 = 2A$$

$$u_3 = 3A$$

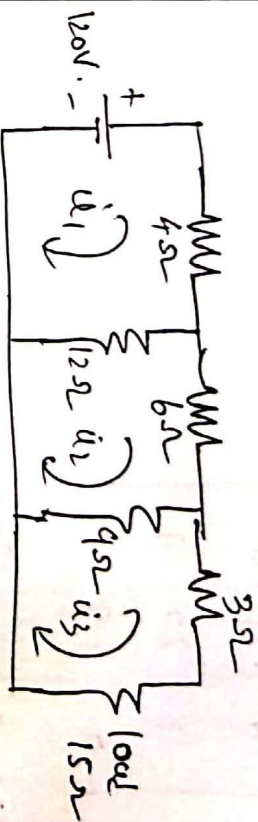3. In the circuit given in figure, obtain the load current and power delivered to the load.



Solution:-
Apply KVL at
Loop

$$4u_1 + 12(u_1 - u_2) = 120$$

$$16u_1 - 12u_2 = 120 \quad \text{--- (1)}$$

$$12(u_2 - u_1) + 6u_2 + 9(u_2 - u_3) = 0$$

$$-12u_1 + 27u_2 - 9u_3 = 0 \quad \text{--- (2)}$$

$$\text{Loops} \quad 9(u_3 - u_2) + 3u_3 + 15u_3 = 0$$

$$-9u_2 + 27u_3 = 0 \quad \text{--- (3)}$$

Matrix representation:-

$$\begin{bmatrix} 16 & -12 & 0 \\ -12 & 27 & -9 \\ 0 & -9 & 27 \end{bmatrix} \begin{bmatrix} u_1 \\ u_2 \\ u_3 \end{bmatrix} = \begin{bmatrix} 120 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 16 & -12 & 0 \\ -12 & 27 & -9 \\ 0 & -9 & 27 \end{vmatrix}$$

$$= 16[729 - 81] + 12[-324 - 0] + 0$$

$$\Delta = 6480$$

$$\Delta_3 = \begin{vmatrix} 16 & -12 & 120 \\ -12 & 27 & 0 \\ 0 & -9 & 0 \end{vmatrix}$$

$$\Delta_3 = 12960$$

$$i_3 = \frac{\Delta_3}{\Delta} = \frac{12960}{6480} = 2A$$

$$u_3 = 2A$$


Current through load resistor 15Ω is $2A$.

So Power delivered to the load is $P = u^2 R$

$$P_s = 60W$$

$$= 2^2 \times 15 = 60W$$

Mesh Equation by Inspection Method:-

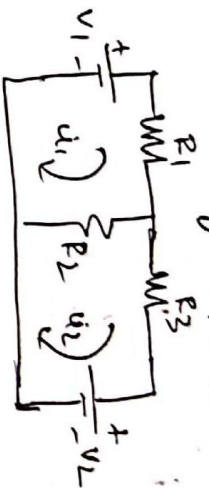

$$\begin{bmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$R_{11} = R_1 + R_2$ (Sum of all resistance in the 1st loop)


$R_{21} = R_{12} = -R_2$ (Total resistance shared by loop

one and two, Negative sign indicates

the current i_1 & i_2 are in opposite direction)

$R_{22} = R_2 + R_3$ (Sum of all the resistances in the 2nd loop)
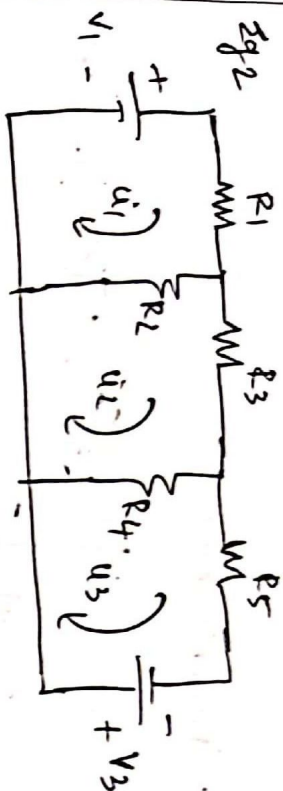
$$\begin{bmatrix} R_{11} + R_2 & -R_2 \\ -R_2 & R_2 + R_3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ -V_2 \end{bmatrix}$$




$$\begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$\begin{bmatrix} R_1 + R_2 & -R_2 & 0 \\ -R_2 & R_2 + R_3 + R_4 & -R_4 \\ 0 & -R_4 & R_4 + R_5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ 0 \\ V_3 \end{bmatrix}$$

Problem:

1. Find the current through 8Ω resistor

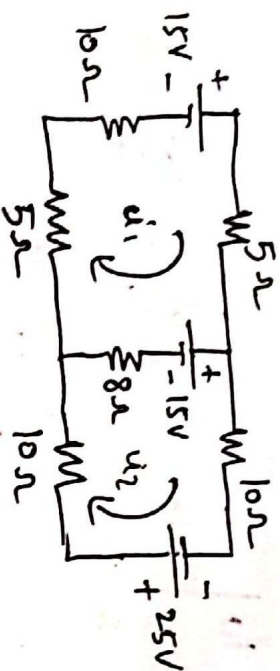

Solution by using mesh inspection method.

$$\begin{bmatrix} R_{11} & -R_{12} \\ -R_{21} & R_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} 5+8+5+10 & -8 \\ -8 & 10+10+8 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 15-15 \\ 15+25 \end{bmatrix}$$

$$\begin{bmatrix} 28 & -8 \\ -8 & 28 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 40 \end{bmatrix}$$

Apply Cramer's rule.

$$\Delta = \begin{vmatrix} 28 & -8 \\ -8 & 28 \end{vmatrix} = 784 - 64 = 720$$

$$\Delta_1 = \begin{vmatrix} 0 & -8 \\ 40 & 28 \end{vmatrix} = 320 \quad I_1 = \frac{\Delta_1}{\Delta} = \frac{320}{720} = 0.44A$$

$$\Delta_2 = \begin{vmatrix} 28 & 0 \\ -8 & 40 \end{vmatrix} = 1120 \quad I_2 = \frac{\Delta_2}{\Delta} = \frac{1120}{720} = 1.55A$$


Current through 8Ω resistor $i_2 - i_1 = 1.55 - 0.44$

$$I_1 = 0.44A$$

$$i_8 = 1.11A$$

$$I_2 = 1.55A$$

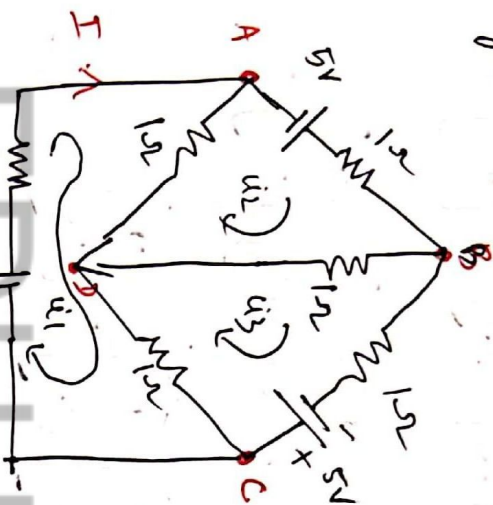2. Determine the currents in bridge circuit by using mesh analysis.



Solution:- By using Inspection method.

$$\begin{bmatrix} R_{11} & -R_{12} & -R_{13} \\ -R_{21} & R_{22} & -R_{23} \\ -R_{31} & -R_{32} & R_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$\begin{bmatrix} 1+1+1 & -1 & -1 \\ -1 & 1+1+1 & -1 \\ -1 & -1 & 1+1+1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 5 \\ 5 \end{bmatrix}$$

By applying Cramer's rule.

$$\Delta = \begin{vmatrix} 3 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{vmatrix} = 3[9-1] + 1[-3-1] - 1[1+3] = 24 - 4 - 1 = 16$$

$$\Delta = 16$$

$$\Delta_1 = \begin{vmatrix} 10 & -1 & -1 \\ 5 & 3 & -1 \\ 5 & -1 & 3 \end{vmatrix} = 120 \quad i_1 = \frac{\Delta_1}{\Delta} = \frac{120}{16} = 7.5A$$

$$i_1 = 7.5A$$

$$\Delta_2 = \begin{vmatrix} 3 & 10 & -1 \\ -1 & 5 & -1 \\ -1 & 5 & 3 \end{vmatrix} = 100 \quad i_2 = \frac{\Delta_2}{\Delta} = \frac{100}{16} = 6.25A$$

$$i_2 = 6.25A$$

$$\Delta_3 = \begin{vmatrix} 3 & -1 & 10 \\ -1 & 3 & 5 \\ -1 & -1 & 5 \end{vmatrix} = 100 \quad i_3 = \frac{\Delta_3}{\Delta} = \frac{100}{16} = 6.25A$$

$$i_3 = 6.25A$$

Current through AD is $i_1 - i_2 = 7.5 - 6.25 = 1.25 \text{ A}$

Current through AB is $i_2 = 6.25 \text{ A}$


Current through BD is $i_2 - i_3 = 6.25 - 6.25 = 0 \text{ A}$

Current through BC is $i_3 = 6.25 \text{ A}$

Current through CD is $i_1 - i_3 = 7.5 - 6.25 = 1.25 \text{ A}$.

Node Method:

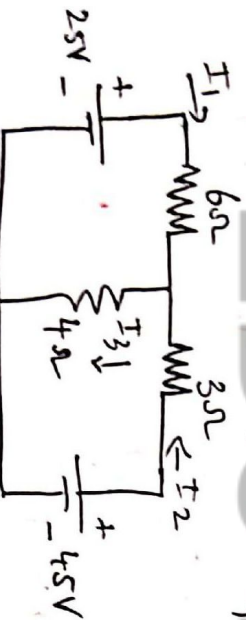
1. Using Node Analysis, obtain the currents flowing in all the resistors of the circuit.



Solution:- Convert all the voltage sources into equivalent sources.

$$I_1 = \frac{25}{6} = 4.166 \text{ A}$$

$$I_2 = 45/3 = 15 \text{ A}$$

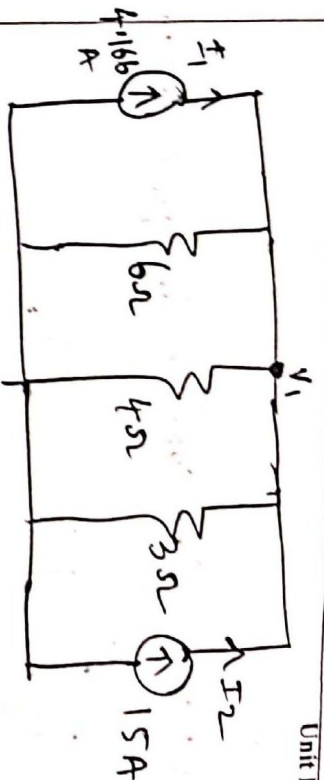

Apply KCL at node V_1

$$4.166 + 15 = \frac{V_1}{6} + \frac{V_1}{4} + \frac{V_1}{3}$$

$$19.166 = V_1 \left[\frac{1}{6} + \frac{1}{4} + \frac{1}{3} \right]$$

$$19.166 = V_1 [0.75]$$

$$V_1 = \frac{19.166}{0.75} = 25.55 \text{ V}$$

$$V_1 = 25.55 \text{ V}$$

Current through 6Ω resistor $= \frac{V_1}{6} = \frac{25.55}{6} = 4.25 \text{ A}$

Current through 4Ω resistor $= \frac{V_1}{4} = \frac{25.55}{4} = 6.38 \text{ A}$

Current through 3Ω resistor $= \frac{V_1}{3} = \frac{25.55}{3} = 8.51 \text{ A}$

2. Using Nodal Method Find Current through 8Ω resistor




Convert all the voltage sources in to equivalent current sources.

$$I_1 = 4/5 = 0.8 \text{ A}$$

$$I_2 = 6/12 = 0.5 \text{ A}$$

Circuit becomes

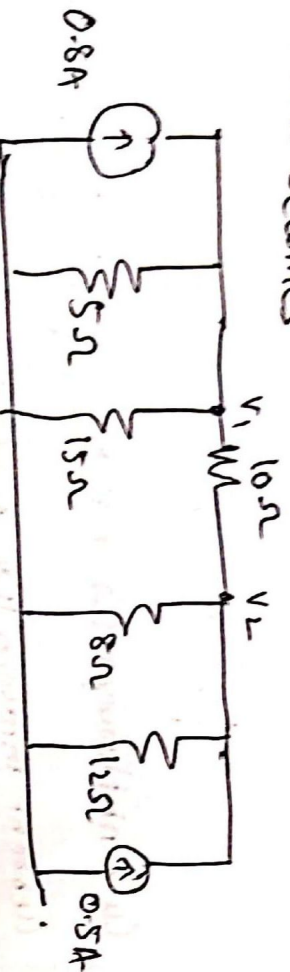

Matrix form by inspection method.

$$\begin{bmatrix} \frac{1}{5} + \frac{1}{15} + \frac{1}{10} & -\frac{1}{10} \\ -\frac{1}{10} & \frac{1}{10} + \frac{1}{8} + \frac{1}{12} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 0.8 \\ 0.5 \end{bmatrix}$$

$$\begin{bmatrix} 0.366 & -0.1 \\ -0.1 & 0.308 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 0.8 \\ 0.5 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 0.366 & -0.1 \\ -0.1 & 0.308 \end{vmatrix} = 0.112 - 0.01$$

$$\Delta = 0.102$$

$$\Delta V_1 = \begin{vmatrix} 0.8 & -0.1 \\ 0.5 & 0.308 \end{vmatrix} = 0.2464$$

$$\Delta V_2 = \begin{vmatrix} 0.366 & 0.8 \\ -0.1 & 0.5 \end{vmatrix} = 0.263$$


$$V_1 = \frac{\Delta V_1}{\Delta} = \frac{0.2464}{0.102} = 2.405 \text{ V}$$

$$V_2 = \frac{\Delta V_2}{\Delta} = \frac{0.263}{0.102} = 2.578 \text{ V}$$

$$V_L = 2.578 \text{ V}$$

Current through 8Ω resistor = $\frac{V_2}{8} = \frac{2.578}{8} = 0.322 \text{ A}$

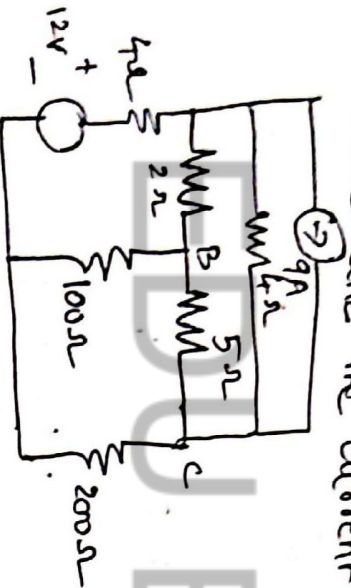
3. Use Nodal Analysis to determine the voltage across 5Ω resistance and the current in the 12 V source.



Solution:- Convert voltage source into current source.

$$I = V/R = 12/4 = 3 \text{ A}$$

Circuit becomes.

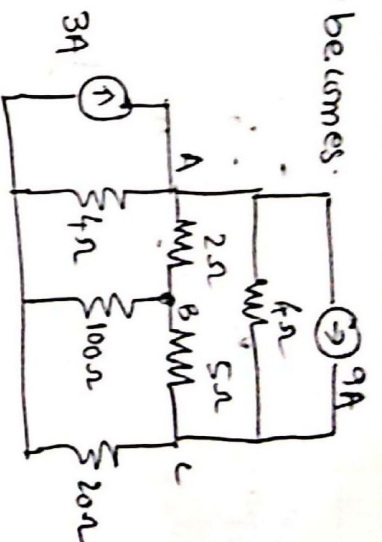

At node A, the current is $3 - 9 = -6 \text{ A}$

At node B, the current is zero.

At node C, the current is 9 A

Note Equation in matrix form

$$\begin{bmatrix} \frac{1}{4} + \frac{1}{2} + \frac{1}{4} & -\frac{1}{2} & -\frac{1}{4} \\ -\frac{1}{2} & \frac{1}{2} + \frac{1}{100} + \frac{1}{5} & -\frac{1}{5} \\ -\frac{1}{4} & -\frac{1}{5} & \frac{1}{5} + \frac{1}{20} + \frac{1}{4} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} -6 \\ 0 \\ 9 \end{bmatrix}$$

$$\begin{bmatrix} 1 & -0.5 & -0.25 \\ -0.5 & -0.71 & -0.2 \\ -0.25 & -0.2 & 0.5 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} -6 \\ 0 \\ 9 \end{bmatrix}$$

Solve V_B & V_C

$$\Delta = \begin{vmatrix} 1 & -0.5 & -0.25 \\ -0.5 & -0.71 & -0.2 \\ -0.25 & -0.2 & 0.5 \end{vmatrix}$$

$$\Delta = 0.0956$$

$$= (0.355 - 0.04) + 0.5(-0.254 - 0.05) - 0.25(0.1 + 0.175)$$

$$\Delta V_B = \begin{vmatrix} 1 & -6 & -0.25 \\ -0.5 & 0 & -0.2 \\ -0.25 & 9 & 0.5 \end{vmatrix}$$

$$= 1.125$$

$$\Delta V_B = 1.125$$

$$V_B = \frac{\Delta V_B}{\Delta} = \frac{1.125}{0.0956} = \underline{\underline{11.76V}}$$

$$V_B = 11.76V$$

$$\Delta V_C = \begin{vmatrix} 1 & -0.5 & -6 \\ -0.5 & -0.71 & 0 \\ -0.25 & -0.2 & 9 \end{vmatrix}$$

$$= 2.475$$

$$\Delta V_C = 2.475$$


$$V_C = \frac{\Delta V_C}{\Delta} = \frac{2.475}{0.0956} =$$

$$V_C = \underline{\underline{25.88V}}$$

Voltage across 5Ω is $V_B - V_C$

$$= 11.76 - 25.88$$

$$V_{5\Omega} = \underline{\underline{-14.12V}}$$

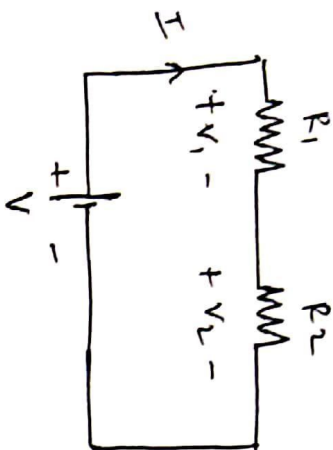
Voltage Division rule:-

If two resistors are connected in series and if the total voltage applied is V , then the voltage across any one resistance can be found by using the formula

$$= \frac{\text{total voltage} \times \text{same Resistance in which voltage need to be found}}{\text{Sum of the Resistance.}}$$

$$V_1 = \frac{V \times R_1}{R_1 + R_2}$$

$$V_2 = \frac{V \times R_2}{R_1 + R_2}$$

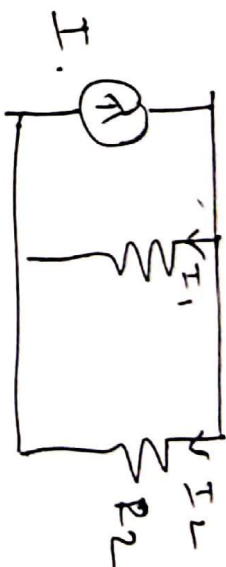Current Division Rule:-

If two resistors are connected in parallel and the total current entering the parallel combination is known, then the current flowing through the resistors can be calculated using

$$\frac{\text{total current} \times \text{opposite Resistance}}{\text{Sum of the Resistance.}}$$

$$I_1 = \frac{I \times R_2}{R_1 + R_2}$$

$$I_2 = \frac{I \times R_1}{R_1 + R_2}$$



EDU ***ENGINEERING***

PIONEER OF ENGINEERING NOTES

CONNECT WITH US



WEBSITE: www.eduengineering.in



TELEGRAM: [@eduengineering](https://t.me/eduengineering)

- Best website for **Anna University Affiliated College** Students
- Regular Updates for all Semesters
- All **Department Notes** AVAILABLE
- All **Lab Manuals** AVAILABLE
- **Handwritten** Notes AVAILABLE
- **Printed** Notes AVAILABLE
- **Past Year** Question Papers AVAILABLE
- Subject wise **Question Banks** AVAILABLE
- Important Questions for Semesters AVAILABLE
- Various Author Books AVAILABLE

