



EDU ***ENGINEERING***

PIONEER OF ENGINEERING NOTES

CONNECT WITH US




WEBSITE: www.eduengineering.in




TELEGRAM: [@eduengineering](https://t.me/eduengineering)

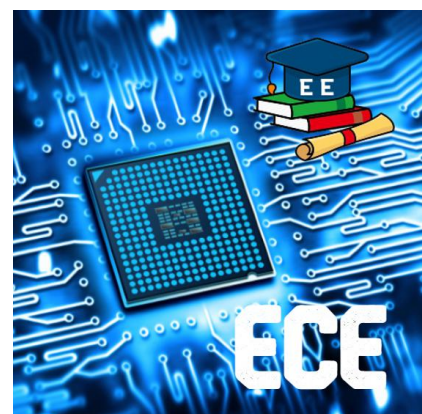- Best website for **Anna University Affiliated College** Students
- Regular Updates for all Semesters
- All **Department Notes** AVAILABLE
- All **Lab Manuals** AVAILABLE
- **Handwritten** Notes AVAILABLE
- **Printed** Notes AVAILABLE
- **Past Year** Question Papers AVAILABLE
- Subject wise **Question Banks** AVAILABLE
- Important Questions for Semesters AVAILABLE
- Various Author Books AVAILABLE



Super Position Theorem:-

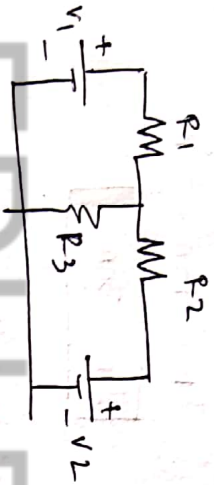Super Position Theorem states that the response in a circuit with multiple sources is given by the algebraic sum of responses due to individual sources acting alone.



Procedure/steps:


- ① In a circuit with multiple sources keep only one source active (V_1 - active, V_2 - short)
- ② Remove all the other sources (voltage sources must be short circuited, current sources must be open circuited)
- ③ Find the response of the circuit for the individual sources and label the term as I_1' , I_2' & I_3' etc.



- ④ Now keep the other source active and remove the first source.



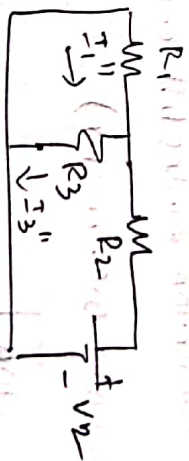- ⑤ Now find the response due to the source V_2 and label the current as I_1'' , I_2'' & I_3'' .



(Follow the same procedure if more than two sources present)

- ⑥ Now find the overall response of the circuit by sum up the individual responses.

$$I_1 = I_1' + I_1''$$

$$I_2 = I_2' + I_2''$$


$$I_3 = I_3' + I_3''$$

[Note: Depending upon the direction assumed sign may vary, once current is calculated other parameters like voltage, power etc can be calculated]

① Find the current through 5Ω resistor using Superposition Theorem.



Step 1: Keep $10A$ Active & Remove $20A$

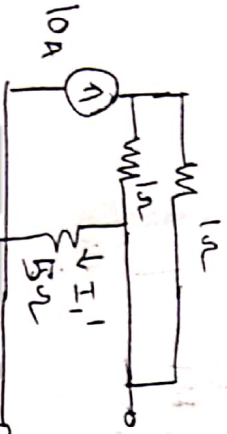

from the fig above current through 5Ω is $10A$

Even though the current $10A$ divides between two 10Ω

it agains join & enter 5Ω resistor)

$$I_{L'} = 10A$$

Step 2: Keep $20A$ Active & Remove $10A$



By inspecting the circuit itself we can observe, the current through 5Ω is $20A$.


$$I_{L''} = 20A$$

So total current through 5Ω resistor $I = I_{L'} + I_{L''}$


$$I = 10A + 20A$$

$$I_L = 30A$$

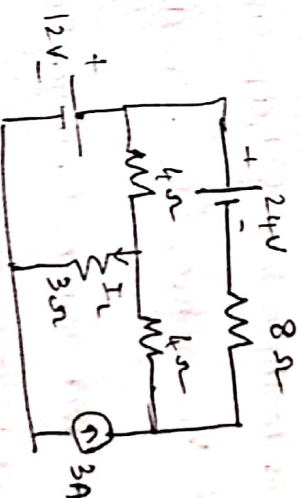② Using Superposition theorem find the current through 3Ω resistor.



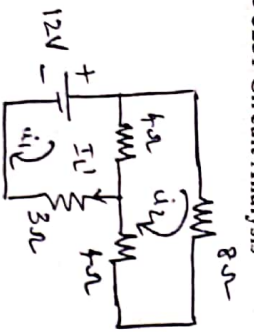Solution: - Keep $12V$ source active $24V$ -short, $3A$ -open circuit.



By KVL

$$-7u_1 + 4u_2 = -12 \quad \text{--- (1)}$$


$$4u_1 - 6u_2 = 0 \quad \text{--- (2)}$$

$$u_1 = 2A$$

$$u_2 = 0.5A$$

So $I_{L1} = 2A$ (since $u_1 = I_{L1}$ in this circuit)

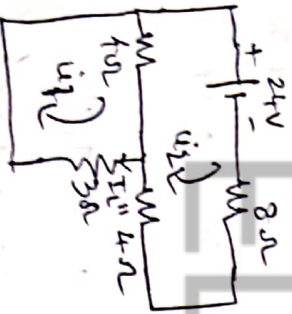Step 2 Keep 24V source active & 12V source short circuited and 3A open circuited.



let I_{L2} be the current through 3A resistor because of the voltage source 24V

$$16u_1 - 4u_2 = -24 \quad \text{--- (1)}$$

$$7u_1 - 4u_2 = 0 \quad \text{--- (2)}$$


$$u_2 = -1.75A$$

$$u_1 = -1A$$

$$I_{L2} = u_2 = -1A$$

$$I_{L2} = -1A$$

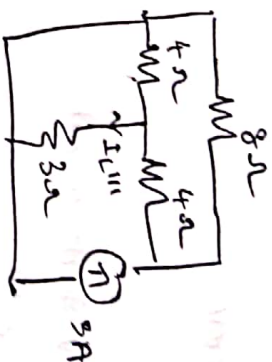Step 3: Keep 12V & 24V source short circuited and 3A source - Active.




let $I_{L3} = I_{3\Omega}$ due to 3A source.

$$4\Omega \parallel 3\Omega = \frac{4 \times 3}{4+3} = 1.714\Omega$$

$$I_{S1} = \frac{3 \times 8}{4+7+4+8} \quad (\text{By current division})$$

$$I_{S1} = 1.887A$$

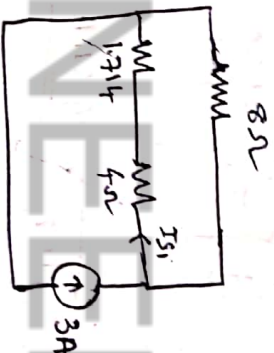

Current division rule.

$$I_{3\Omega} = I_{L3} = \frac{1.887 \times 4}{4+3}$$

$$I_{L3} = 1.078A$$

$$\text{So } I_L = I_{L1} + I_{L2} + I_{L3}$$


$$= 2 - 1 + 1.07 = 3.07A$$

$$I_L = 3.07A$$

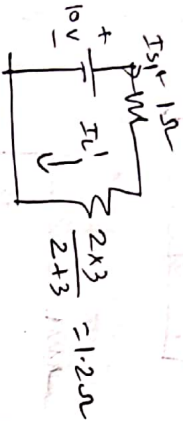
3) Find the current I_L in the circuit using Superposition Theorem



Step 1: keep 10V source active & 20V short circuit.


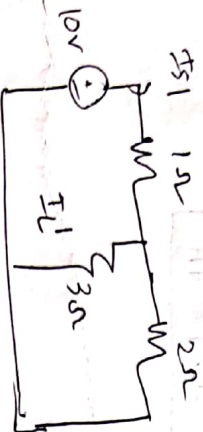
$$I_{S1} = \frac{10}{1+2} = \underline{\underline{4.54A}}$$





2 & 3 Ω are in parallel
So current $I_{L'}$ can be

$$I_{L'} = \frac{I_{S1} \times 2}{2+3} = \frac{4.54 \times 2}{2+3} = \underline{\underline{1.8182A}}$$

Calculated using current division rule.

$$I_{L'} = 1.8182A$$

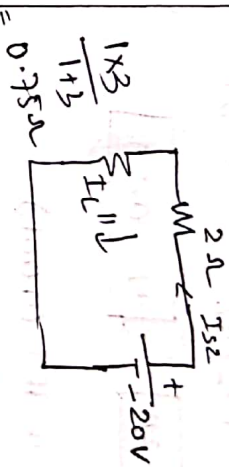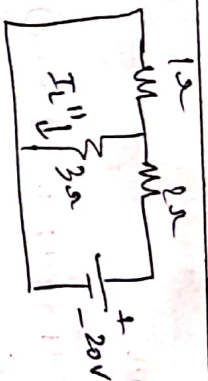

$$I_{S2} = \frac{20}{1+2} = 0.75A$$

$$I_{S2} = \frac{20}{2+0.75} = 7.27A$$



$$I_{L''} = I_{S2} \times \frac{1}{1+3}$$

$$I_{S2} = \frac{20}{2+0.75} = 7.27A$$

$$I_{L''} = 1.818A$$

$$I_{L''} = I_{S2} \times \frac{1}{1+3}$$

$$I_L = I_{L'} + I_{L''}$$

$$= 1.8182 + 1.8182$$

$$I_L = 3.6364A$$

Thvenin's Theorem:-

Thvenin's Theorem states that a circuit with two terminals can be replaced with an equivalent circuit consisting of a voltage source in series with a resistance or impedance.

Steps:

Step 1: Calculate R_{th} (Thvenin's equivalent resistance)

Step 1: Remove the load resistor

Step 2: Remove all the voltage sources (short circuit)

Step 3: Remove all the current sources (open circuit)

Step 4: Measure the Resistance across the load terminals, which is the Thvenin's resistance (R_{th})

Steps to calculate V_{th} (Thvenin's equivalent voltage)

Step 1: Remove the load resistor and then measure the voltage drop across the load terminal, which gives the open circuit voltage also called Thvenin's voltage


Step 3: To calculate the current through load resistance use the formula.

$$I_L = V_{th} / R_{th} + R_L$$



Replace the circuit as shown above & find I_L .

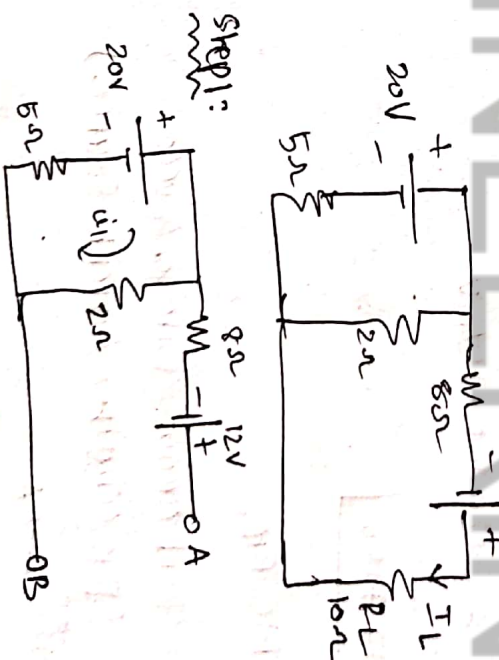Problem: Determine the current I_L using Thvenin's theorem.



$$2u_1 + 5u_2 = 20$$


$$u_1 = 20/3 = 2.857A$$

Voltage across 2Ω resistor

$$V_{2\Omega} = I_{2\Omega} \times R = 2.85 \times 2$$

$$V_{2\Omega} = 5.714V$$

12V voltage source is added

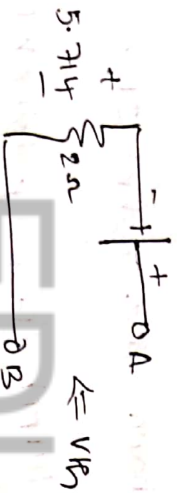


$$V_{th} = 12V + 5.714V = 17.714V$$

$$V_{th} = 17.714V$$

Step 2 To calculate R_{th}

Remove load, short circuit - voltage source

Open circuit - current source

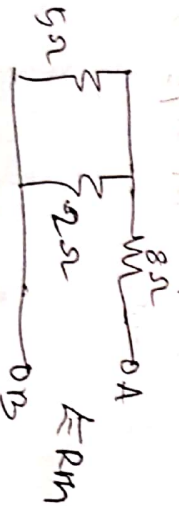

$$R_{th} = 8 + \frac{5 \times 2}{5+2} = 8 + 1.428 = 9.428\Omega$$

$$R_{th} = 9.428\Omega$$

Step 3 To calculate load current I_L

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$


$$I_L = \frac{17.714}{9.428 + 10} = 0.9118A$$


$$I_L = 0.9118A$$

② Using Thevenin's theorem find the current I_L in the circuit.



To find V_{th} .

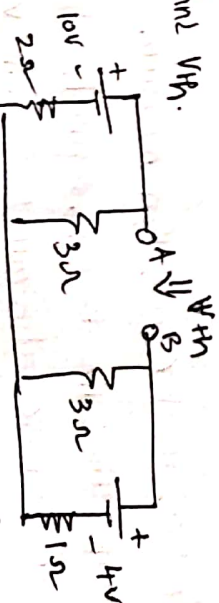

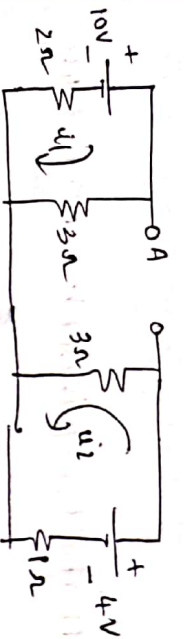

loop 1

$$3u_1 + 2u_1 = 10$$

$$5u_1 = 10$$

$$u_1 = 2A$$


loop 2

$$3u_2 + u_2 = 4$$

$$4u_2 = 4$$

$$u_2 = 1A$$

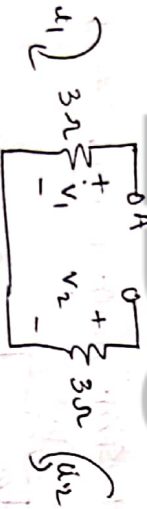
To find voltage drop across A & B, we need to find voltage drop across both the 3Ω resistors.



$$\text{Voltage } V_1 = u_1 \times 3 = 2 \times 3 = 6V$$

$$V_2 = u_2 \times 3 = 1 \times 3 = 3V$$

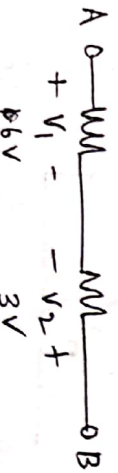Redraw the circuit for better understanding




$$\text{So } V_{AB} = V_{th} = 6V - 3V = 3V$$

$$V_{th} = 3V$$

To find Thevenin's Resistance R_{th}



Redraw the circuit.

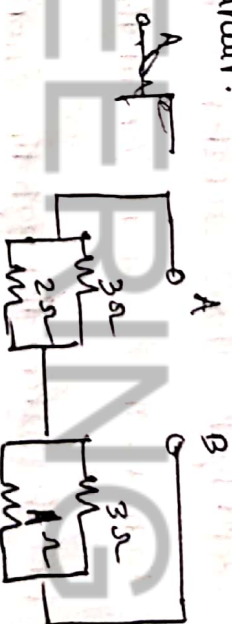


$$R_{th} = \left(\frac{3 \times 2}{3+2} \right) + \left(\frac{3 \times 1}{3+1} \right)$$

$$R_{th} = 1.95\Omega$$

Thevenin's circuit:

$$R_{th} = 1.95\Omega$$

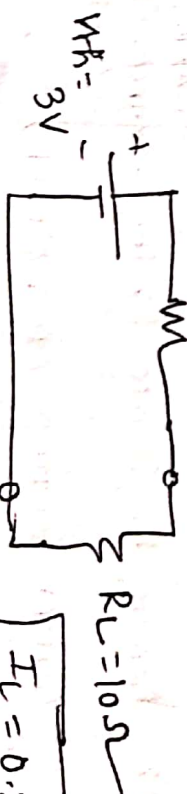

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{3}{1.95 + 10}$$

$$= 0.251A$$

$$I_L = 0.251A$$

Norton's Theorem:

States that it is possible to simplify any linear circuit to an equivalent circuit with just a single current source and parallel resistance connected to a load.

Steps: To calculate Norton's current:-

Step 1: Identify the load resistor.

Step 2: Remove it & short circuit the terminals.

Step 3: Find the current through the short circuit terminals which is Norton's current (I_N).

Steps: To calculate R_{th} or R_N (Norton's Resistance)

Step 1: Remove the load resistor (R_L) & label the terminals as A & B



Step 2: Remove the source (voltage source - short circuit source - open circuit)

Step 3: Measure the resistance across the terminals A & B, which gives the Norton's resistance R_N

Step 3: Draw the Norton's equivalent circuit & use the formula


$$I_L = \frac{I_N \cdot R_N}{R_N + R_L}$$

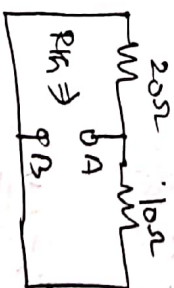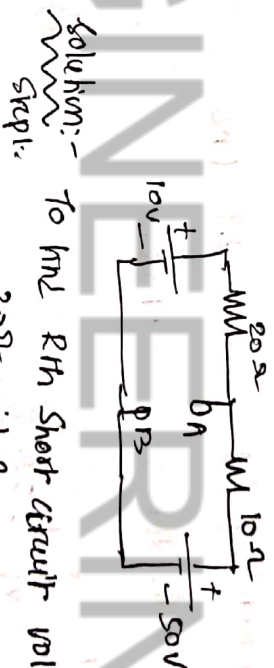Problem:- Find the Thevenin's & Norton's equivalents of the circuit with respect to terminal A & B.



$$R_{th} = \frac{20 \times 10}{20 + 10} = \underline{\underline{6.667 \Omega}}$$

Step 2: To find V_{th}

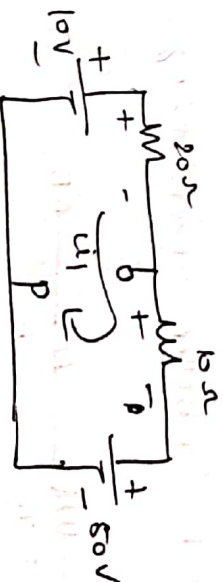


$$20i_1 + 10i_1 + 50 - 10 = 0$$

$$30i_1 = -40$$


$$i_1 = -40/30 = -1.33A$$

$$i_1 = -1.33A$$

Voltage across A & B is either

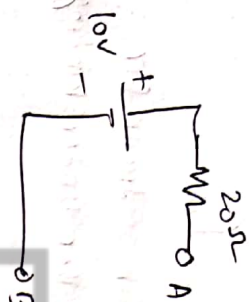

(or)

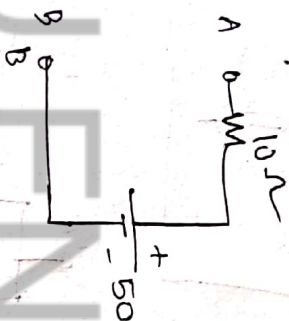

We select LHS


$$V_{AB} = 10V - \text{Voltage across } 20\Omega$$

$$V_{20\Omega} = i_1 \times 20 = -26.66V$$


$$V_H = V_{AB} = 10 - (-26.66V)$$

$$V_H = 36.66V$$

Thevenin's circuit:-

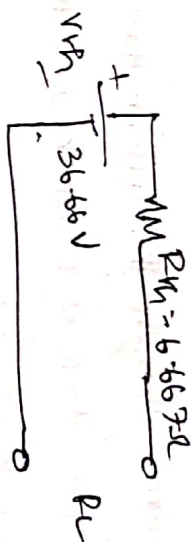

for Norton's Theorem:

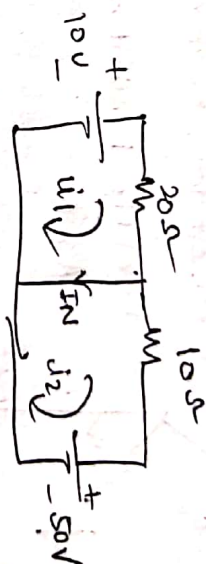

loop 1

$$20i_1 = 10$$

$$i_1 = 0.5A$$

loop 2


$$10i_2 + 50 = 0$$

$$i_2 = -5A$$


$$I_N = i_1 - i_2$$

$$= 0.5 - (-5) = I_N = 5.5A$$

Norton's equivalent ckt:

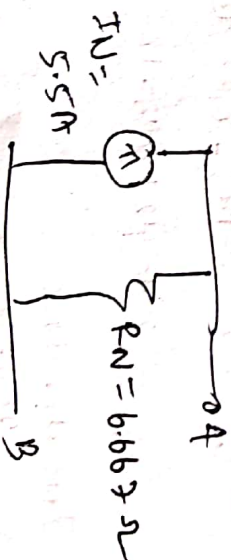


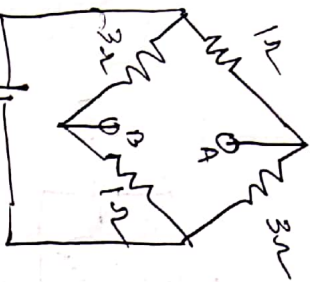② Using Norton's theorem, determine the current through an ammeter connected across A & B of the circuit, take the resistance of the ammeter as 0.5Ω



1. Remove load resistor & label the terminals A & B.

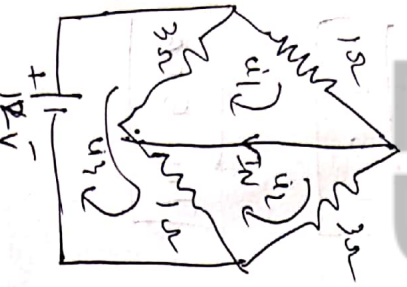2. Short circuit the terminal A & B and find the current through it



$$i_1 + 3i_1 - 3i_3 = 0 \text{ --- (1)}$$

$$4i_1 - 3i_3 = 0 \text{ --- (1)}$$

$$4i_2 - 1i_3 = 0 \text{ --- (2)}$$

$$-3i_1 - i_2 + 4i_3 = 12 \text{ --- (3)}$$

$$I_N = i_1 - i_2$$

$$= 6 - 2 = 4A$$


$$i_1 = 6A$$

$$i_2 = 2A$$

$$i_3 = 8A$$

$$I_N = 4A$$


To find R_{th} or R_N

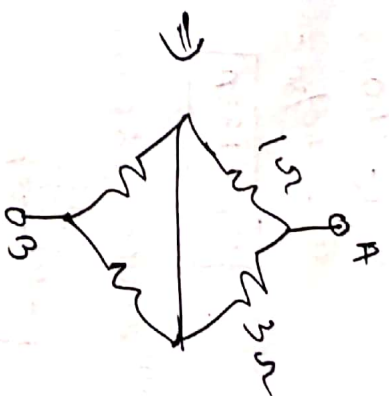

Circuit is drawn for better understanding

$$R_N = 1.5\Omega$$

Norton's equivalent circuit:

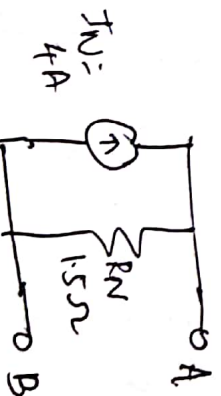

Maximum Power Transfer Theorem (MPT)

MPT states that maximum power will be delivered to the load when the load impedance and source impedance are equal.


Steps:

- ① Find R_{th} (Remove voltage source; current source & load resistance & label the terminals as A & B)
- ② find the V_{th} (Thevenin's equivalent voltage) i.e. the voltage across the terminals A & B.
- ③ find maximum power using the formula.

$$P_{max} = \frac{V_{th}^2}{4R_{th}}$$

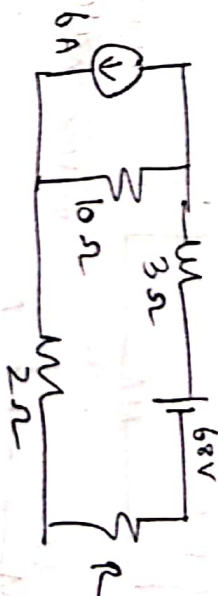
Problems:

- ① find the value of 'R' for maximum power transfer and calculate the maximum power.




Soln

Step 1:- find R_{th} (Remove E_1)

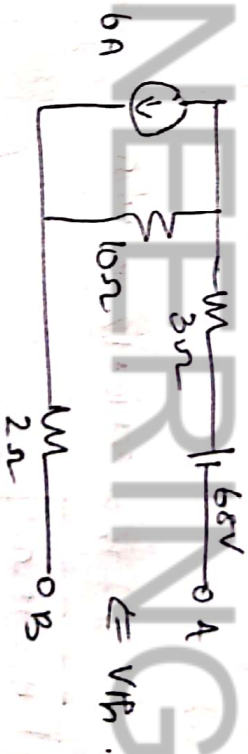

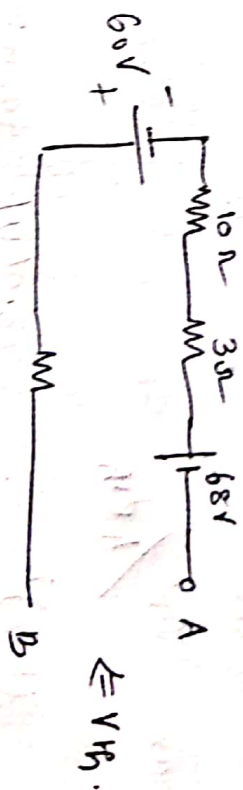
$V = IR$ (By source transformation formula)



6V & 6V are in series

So $V_{th} = 12V$

Step 2. To find R_{Th}

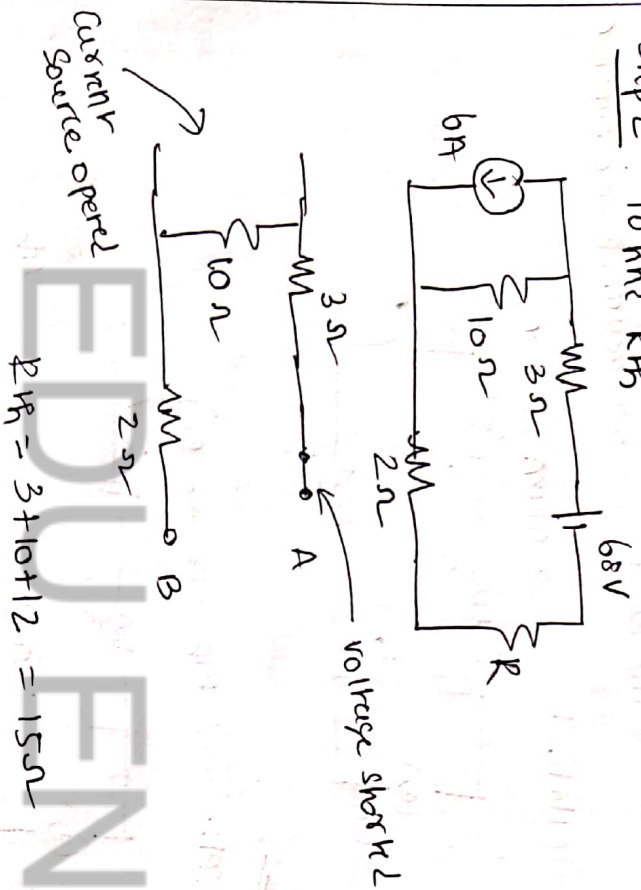

$$R_{Th} = 15\Omega$$


Maximum Power P_{max}

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}}$$

$$= \frac{(128)^2}{4 \times 15} = 273.06W$$

$$P_{max} = 273.06W$$

$$R_{Th} = R_L = 15\Omega$$

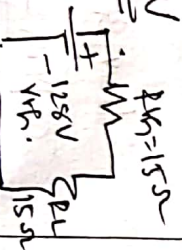

Reciprocity Theorem:

The Reciprocity Theorem states that in a linear bilateral, single source circuit, the ratio of excitation to response is constant, when the position of the excitation and response are interchanged.

Steps:-

1. Interchange the position of source & response.

[Voltage - short]
[Current - open]


2. Find the Response at the particular branch.

Before

3. Compare it with the response before interchanging.

that you got

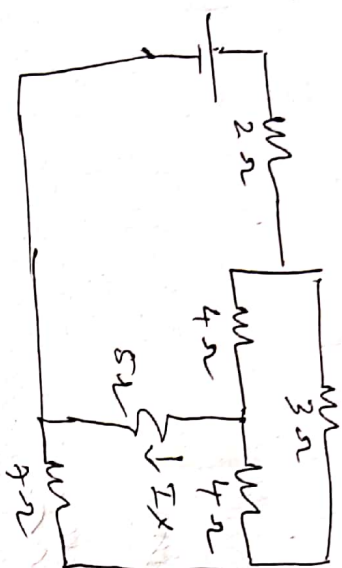1. Calculate I_X from the reciprocity theorem by interchanging the position of the source & I_X .



Soln:

Interchanging source & response.



$$\begin{bmatrix} 2+4+5 & -5 & -4 \\ -5 & 5+4+7 & -4 \\ -4 & -4 & 3+4+4 \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 10 \\ -11 \\ 0 \end{bmatrix}$$

$$\Delta = 1069$$


$$\Delta_a = \begin{bmatrix} 10 & -5 & -4 \\ -10 & 16 & -4 \\ 0 & -4 & 11 \end{bmatrix} = 890$$

$$I_X = I_a = \frac{\Delta_a}{\Delta} = \frac{890}{1069}$$

$$I_X = I_a = \frac{\Delta_a}{\Delta} = \frac{890}{1069} = 0.8326A$$

$$I_X = I_a = 0.8326A$$

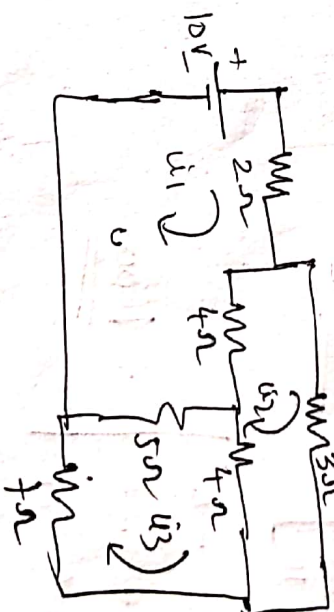for original circuit (original position of the voltage source)




$$I_X = I_1 - I_2$$

$$Z_{eq} = \frac{1}{\frac{1}{z_1} + \frac{1}{z_2} + \dots + \frac{1}{z_n}}$$

$$E_{eq} = \left[\frac{E_1}{z_1} + \frac{E_2}{z_2} + \frac{E_3}{z_3} + \dots + \frac{E_n}{z_n} \right] Z_{eq}$$

Problem:-

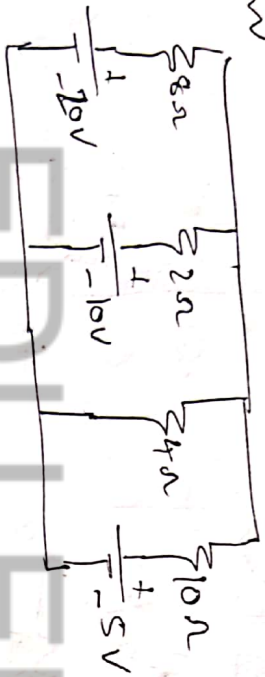

Soln Re-arranging the circuit.




$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{1}{\frac{1}{8} + \frac{1}{2} + \frac{1}{10}}$$

$$R_{eq} = 1.3793 \Omega$$

$$E_{eq} = \left[E_1/R_1 + E_2/R_2 + E_3/R_3 \right] \cdot R_{eq}$$

$$= \left[\frac{20}{8} + \frac{10}{2} + \frac{5}{10} \right] \times 1.3793$$

$$E_{eq} = 11.0344 \text{ V}$$

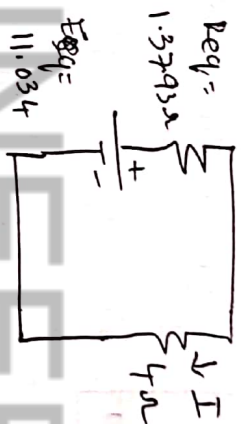


$$V = IR$$

$$I = V/R$$

$$= \frac{11.0344}{(1.3793 + 4)}$$

$$I = 2.0513 \text{ A}$$

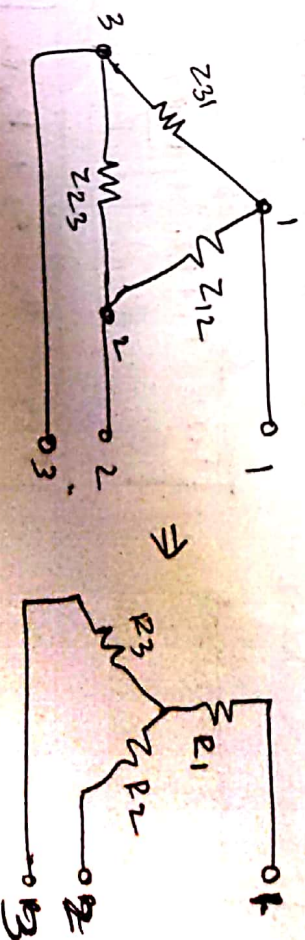Impedance in star to delta (Δ & Delta to star




$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$R_2 = \frac{R_{12} R_{23}}{R_{12} + R_{23} + R_{31}}$$


$$R_3 = \frac{R_{23} R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$R_3 = \frac{R_{23} R_{31}}{R_{12} + R_{23} + R_{31}}$$

Star to Delta:

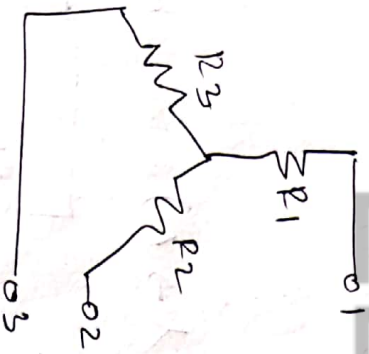

$\Rightarrow$

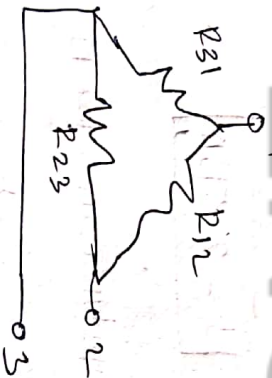


$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$


$$R_{31} = R_3 + R_1 + \frac{R_3 R_1}{R_2}$$

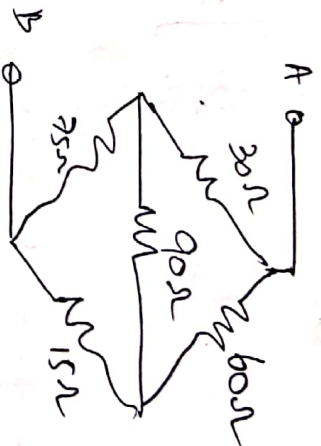Problem:

Find the equivalent resistance of the network.




Soln

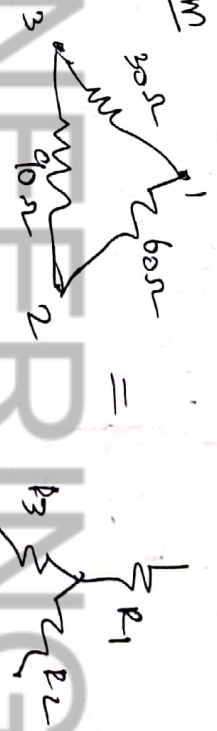


$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}} = \frac{60 \times 30}{30 + 90 + 60} = \underline{\underline{10 \Omega}}$$

$$R_2 = \frac{R_{12} R_{23}}{R_{12} + R_{23} + R_{31}} = \frac{60 \times 90}{30 + 90 + 60} = \underline{\underline{30 \Omega}}$$
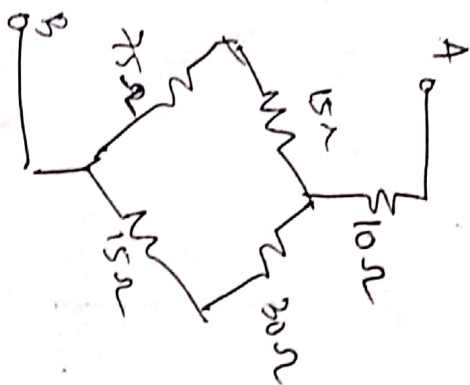
$$R_3 = \frac{R_{31} R_{23}}{R_{12} + R_{23} + R_{31}} = \frac{30 \times 90}{30 + 90 + 60} = \underline{\underline{15 \Omega}}$$




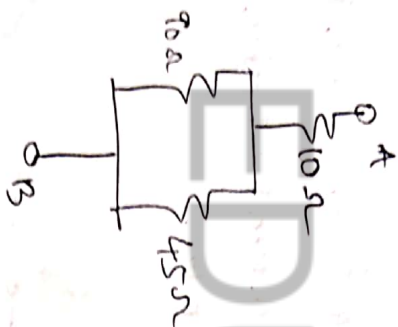15Ω & 75Ω are in series
30Ω & 15Ω are in series




90 & 45 are in
Parallel.
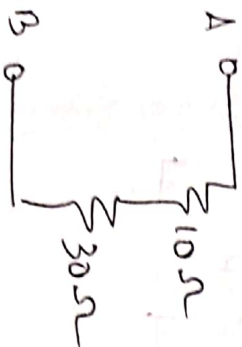
$$90 \parallel 45 = \underline{\underline{30\Omega}}$$




$$R_{AB} = 40\Omega$$

Duality:

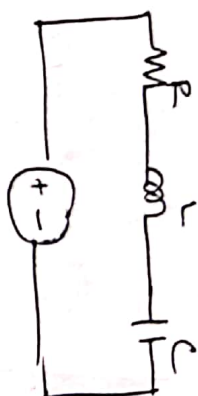

Original network

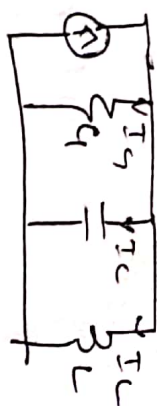

Dual Network

* In an electrical network, electrical terms are associated in to pairs called as duals.


* A dual of a expression is formed by interchanging voltage & current in the expressions

Dual Elements.


original	dual
Resistance	Conductance
Capacitance	Inductance
Inductance	Capacitance
Voltage source	Current source

Original	Dual
Current source	Voltage source.
Series Branch	Parallel Branch
Mesh equation	Node equation
KCL	KVL
Switch closed at $t=0$	Switch opened at $t=0$.
Open circuit	Short circuit
Short circuit	Open circuit
Impedance	Admittance.
Reactance	Susceptance.

Draw the dual of the network shown.

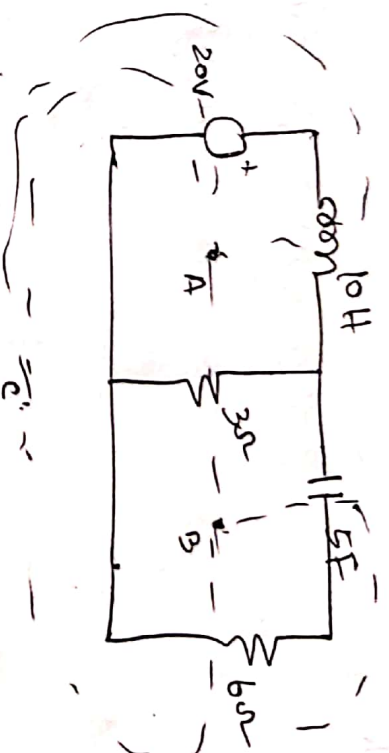

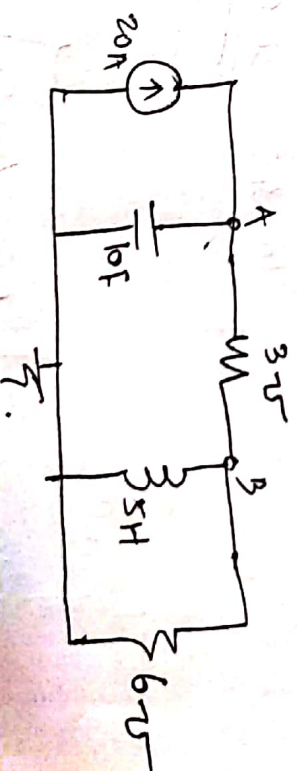- ① Label A & B inside loops & place reference node outside
- ② Draw a dotted line from each node to reference node through all the available branches.
- ③ Draw its Dual.





EDU ***ENGINEERING***

PIONEER OF ENGINEERING NOTES

CONNECT WITH US



WEBSITE: www.eduengineering.in



TELEGRAM: [@eduengineering](https://t.me/eduengineering)

- Best website for **Anna University Affiliated College** Students
- Regular Updates for all Semesters
- All **Department Notes** AVAILABLE
- All **Lab Manuals** AVAILABLE
- **Handwritten** Notes AVAILABLE
- **Printed** Notes AVAILABLE
- **Past Year** Question Papers AVAILABLE
- Subject wise **Question Banks** AVAILABLE
- Important Questions for Semesters AVAILABLE
- Various Author Books AVAILABLE

