



EDU ***ENGINEERING***

PIONEER OF ENGINEERING NOTES

CONNECT WITH US




WEBSITE: www.eduengineering.in



TELEGRAM: [@eduengineering](https://t.me/eduengineering)

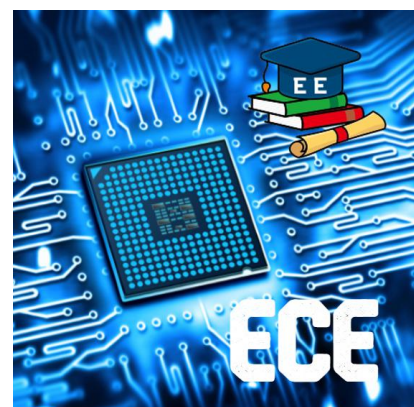- Best website for **Anna University Affiliated College** Students
- Regular Updates for all Semesters
- All **Department Notes** AVAILABLE
- All **Lab Manuals** AVAILABLE
- **Handwritten** Notes AVAILABLE
- **Printed** Notes AVAILABLE
- **Past Year** Question Papers AVAILABLE
- Subject wise **Question Banks** AVAILABLE
- Important Questions for Semesters AVAILABLE
- Various Author Books AVAILABLE




Sinusoid $\rightarrow$ is a signal that has the form of the cosine or sine function.

$$v(t) = V_m \sin \omega t$$

V_m = amplitude of the sinusoid.

ω = angular frequency in radians

ωt = the argument of the sinusoid.

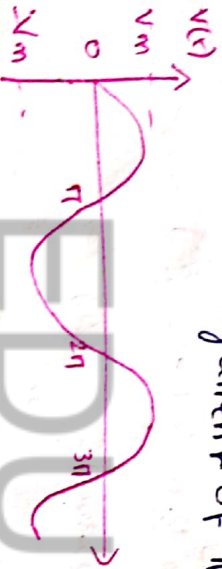

$$\omega T = 2\pi$$

$$T = \frac{2\pi}{\omega}$$

T = Period of sinusoid.

$$f = 1/T$$

$$\omega = 2\pi f$$

f = frequency in hertz $\Rightarrow$ or


f' is also called cycle frequency.

ω = angular frequency.

More general expression for the sinusoid.

$$v(t) = V_m \sin(\omega t + \phi)$$

ϕ = phase.

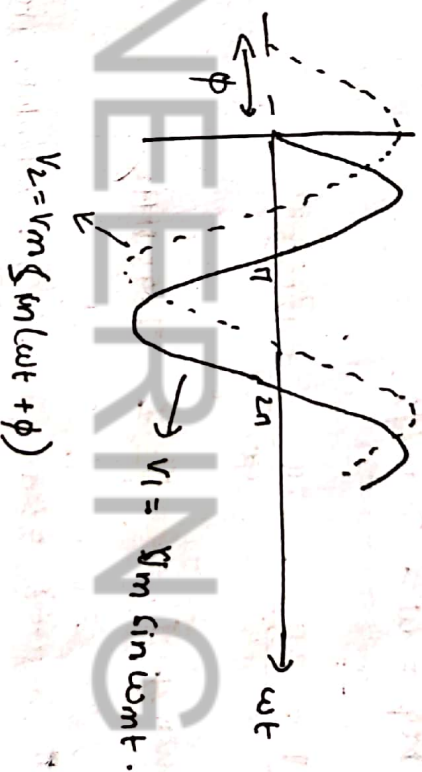

$$v_2 = V_m \sin(\omega t + \phi)$$

The starting point of v_2 occurs first in time, therefore

we say that v_2 leads v_1 by ϕ (or) v_1 lags v_2 by ϕ

If $\phi = 0 \Rightarrow v_1$ & v_2 are in-phase.

$\phi \neq 0 \Rightarrow v_1$ & v_2 are out-of-phase.

① Find the amplitude, phase & frequency of the sinusoid.

$$V(t) = 12 \cos(50t + 10^\circ)$$

$$\text{Amplitude} = V_m = 12 \text{ V}$$

$$\text{Phase} = \phi = 10^\circ$$

$$\text{Angular freq} = \omega = 50 \text{ rad/s}$$

$$\text{Period } T = \frac{2\pi}{\omega} = \frac{2\pi}{50} = 0.1257 \text{ s}$$

$$\text{Frequency } f = \frac{1}{T} = 7.958 \text{ Hz}$$

② Given the sinusoid $5 \sin(4\pi t - 60^\circ)$, calculate its

amplitude, phase, angular frequency, period and frequency.

$$\text{Amplitude} = 5 \text{ V}$$

$$\text{Phase} = -60^\circ$$

$$\text{Angular frequency } \omega = 4\pi = 4 \times 3.14 = 12.56 \text{ rad/sec}$$

$$\text{frequency } f = \frac{\omega}{2\pi} = \frac{12.56}{2 \times \pi} = \underline{\underline{2 \text{ Hz}}}$$

① Calculate the phase angle between $V_1 = -10 \cos(\omega t + 50^\circ)$ and

$V_2 = 12 \sin(\omega t - 10^\circ)$ state which sinusoid is leading.

$$V_1 = -10 \cos(\omega t + 50^\circ)$$

$$= 10 \cos(\omega t + 50^\circ - 180^\circ)$$

$$= 10 \cos(\omega t - 130^\circ) \quad (\text{or}) \quad 10 \cos(\omega t + 230^\circ)$$

$$V_2 = 12 \sin(\omega t - 10^\circ) = 12 \cos(\omega t - 10^\circ - 90^\circ)$$

$$V_2 = 12 \cos(\omega t - 100^\circ) \quad \text{--- ②}$$

from ① & ② Phase difference between V_1 & V_2 is 30° .

V_2 leads V_1 by 30° .

Phasors:

A Phasor is a complex number that represents the amplitude and phase of a sinusoid.

Rectangular form.

$$Z = x + jy$$

Complex no. in rectangular form.

$$j = \sqrt{-1}$$

$x \Rightarrow$ real part

$y \Rightarrow$ imaginary part

Complex no. can also be written in polar form.

Polar form:

$$Z = r \angle \phi = r e^{j\phi}$$

Complex no. 'Z' can also be written in polar or exponential form.

$r =$ magnitude of 'Z'

$\phi =$ phase of Z

$Z = x + jy \Rightarrow$ Rectangular form

$Z = r \angle \phi \Rightarrow$ Polar form

$Z = r e^{j\phi} \Rightarrow$ Exponential form.

Addition & Subtraction are better performed in Rectangular form.

Multiplication & Division are better performed in Polar form

Addition:

$$Z_1 + Z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

Subtraction:

$$Z_1 - Z_2 = (x_1 - x_2) + j(y_1 - y_2)$$

Multiplication:

$$Z_1 Z_2 = r_1 r_2 \angle \phi_1 + \phi_2$$

Division:

$$\frac{Z_1}{Z_2} = \frac{r_1}{r_2} \angle \phi_1 - \phi_2$$

Reciprocal:

$$1/z = 1/z \angle -\phi$$

Squareroot


$$\sqrt{z} = \sqrt{r} \angle \phi/2$$

Complex conjugate:

$$z^* = x - jy = r \angle -\phi = r e^{-j\phi}$$

$$v(t) = V_m \cos(\omega t + \phi) = \text{Time Domain representation}$$

$$V = V_m \angle \phi = \text{Phasor domain representation}$$

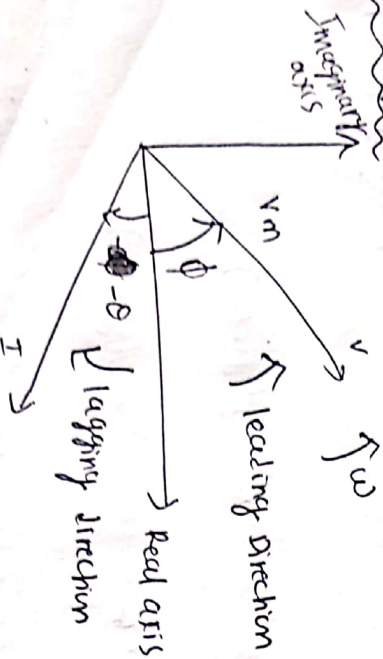Phasor Diagram:Phasor Diagram Drawing:

$$V = V_m \angle \phi \quad \& \quad I = I_m \angle -\theta$$

Problems:

Transform the sinusoids to phasors.

$$① \quad i = 6 \cos(50t - 40^\circ) \text{ A}$$

$$I = 6 \angle -40^\circ \text{ A}$$

$$② \quad v = -4 \sin(30t + 150^\circ) \text{ V}$$

$$= 4 \cos(30t + 150^\circ + 90^\circ)$$

$$= 4 \cos(30t + 140^\circ) \text{ V}$$

$$\left(\begin{array}{l} \text{Since} \\ -\sin A = \cos(A + 90^\circ) \end{array} \right)$$

$$V = 4 \angle 140^\circ \text{ V}$$

$$③ \quad v = -7 \cos(2t + 40^\circ) \text{ V}$$

$$= 7 \cos(2t + 40^\circ + 180^\circ)$$

$$= 7 \cos(2t + 220^\circ) \text{ V}$$

$$V = 7 \angle 220^\circ \text{ V}$$

(4) $i = 4 \sin(10t + 10^\circ) \text{ A}$


$$= 4 \cos(10t + 10^\circ - 90^\circ) \text{ A}$$

$$= 4 \cos(10t - 80^\circ) \text{ A}$$

$$i = 4 \angle -80^\circ \text{ A}$$

Phasor relationships for circuit elements:-

Resistor

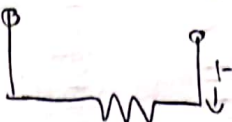

$$i = I_m \cos(\omega t + \phi) = \text{current}$$

$$V = iR$$


$$V = R I_m \cos(\omega t + \phi)$$

Phasor form:-

$$V = R I_m \angle \phi$$


$$I = I_m \angle \phi$$

$$V = IR.$$

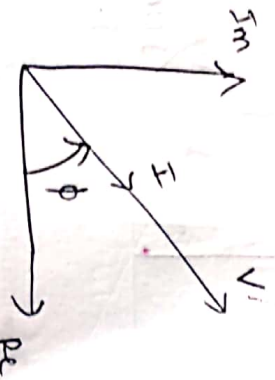


Voltage and current are in-phase.

For Inductor:-

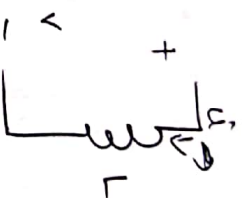

Time domain

$$V = L \frac{di}{dt}$$

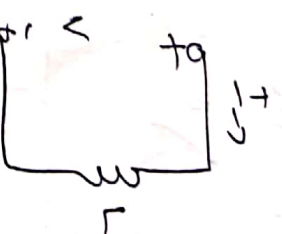

freq. domain

$$V = j\omega L I$$

Assume current through inductor is $i = I_m \cos(\omega t + \phi)$

$$V = L \frac{di}{dt} = -\omega L I_m \sin(\omega t + \phi)$$

~~or~~

$$V = \omega L I_m \cos(\omega t + \phi + 90^\circ)$$


$$V = \omega L I_m \angle \phi + 90^\circ$$

$$I_m \angle \phi = I$$

$$\left[\begin{matrix} \cos \theta = \sin(\theta + 90^\circ) \\ \sin \theta = \cos(\theta - 90^\circ) \end{matrix} \right]$$

$$\left(\begin{matrix} \cos \theta = \sin(\theta + 90^\circ) \\ \sin \theta = \cos(\theta - 90^\circ) \end{matrix} \right)$$

Phasor Diagram for Inductor:-

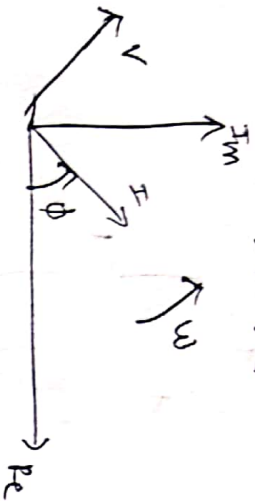


Voltage & current are 90° out of phase.

Current lags voltage by 90° .

For capacitor:-

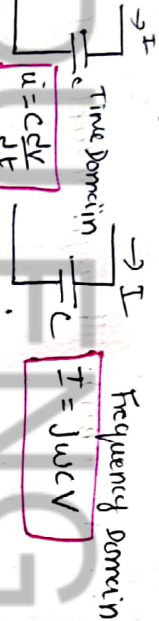
Assume the voltage across it is $v = V_m \cos(\omega t + \phi)$



Current through the capacitor is

$$i = C \frac{dv}{dt}$$
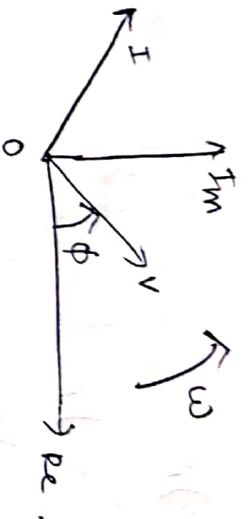
$$I = j\omega C V \Rightarrow V = \frac{I}{j\omega C}$$



Current & voltage are 90° out of phase.

Current leads the voltage by 90° .

Summary of voltage current relationships.

Element	Time Domain	Frequency Domain
R	$V = R i$	$V = R I$
L	$V = L \frac{di}{dt}$	$V = j\omega L I$
C	$i = C \frac{dv}{dt}$	$V = \frac{I}{j\omega C}$

Problem:-

The voltage $V = 12 \cos(60t + 45^\circ)$ is applied to a $0.1H$ Inductor. Find the steady state current through the Inductor.

Soln

$$V = j\omega L I \quad \omega = 60 \text{ rad/s}$$

$$V = 12 \angle 45^\circ \text{ V}$$

$$I = \frac{V}{j\omega L} = \frac{12 \angle 45^\circ}{j60 \times 0.1} = \frac{12 \angle 45^\circ}{6 \angle 90^\circ}$$

$$I = 2 \angle -45^\circ \text{ A}$$

$$I = 2 \cos(60t - 45^\circ) \text{ A}$$

(Time Domain)

If voltage $V = 6 \cos(100t - 30^\circ)$ is applied to a $50\mu F$ capacitor, calculate the current through it.

$$V = \frac{I}{j\omega C}$$

$$I = V j\omega C$$


$$= 6 \angle -30^\circ \times j100 \times 50 \times 10^{-6}$$

$$I = 30 \cos(100t + 60^\circ) \text{ mA}$$

Impedance & Admittance of Passive Elements:-

Element	Impedance	Admittance
R	$Z = R$	$Y = 1/R$
L	$Z = j\omega L$	$Y = 1/j\omega L$
C	$Z = 1/j\omega C$	$Y = j\omega C$

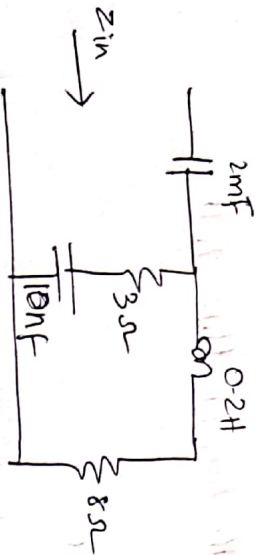Find the input impedance of the circuit; operate at $\omega = 500 \text{ rad/s}$



$$Z_1 = \frac{1}{j\omega C} = \frac{1}{j50 \times 2 \times 10^{-3}} = -j10 \Omega$$

$$Z_2 = 3 + \frac{1}{j\omega C} = 3 + \frac{1}{j50 \times 10 \times 10^{-3}} = (3-j2) \Omega$$

$$Z_3 = 8 + j\omega L = 8 + j50 \times 0.2 = (8 + j10) \Omega$$


Input Impedance

$$Z = Z_1 + Z_2 \parallel Z_3$$

$$= -j10 + \frac{(3-j2)(8+j10)}{11+j8}$$

$$Z_{in} = 3.22 - j11.07 \Omega$$

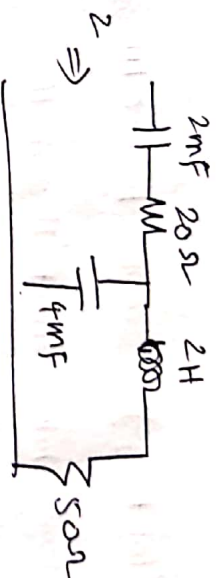Determine the input impedance of the circuit at $\omega = 100 \text{ rad/s}$



$$Z = 32.38 - j73.76 \Omega$$

$$Z_1 = 20 + \frac{1}{j\omega C} = 20 + \frac{1}{j10 \times 2 \times 10^{-3}} = 20 - 50j$$

$$Z_2 = \frac{1}{j\omega C} = \frac{1}{j10 \times 4 \times 10^{-3}} = -25j$$

$$Z_3 = 50 + j\omega L = 50 + j10 \times 2 = 50 + 20j$$


$$Z_1 + (Z_2 \parallel Z_3)$$

$$(20 - 50j) + \frac{(-25j)(50 + 20j)}{(-25j + 50 + 20j)} = \frac{1346.29 \angle -68.19}{50.24 \angle -5.71}$$

$$= 53.85 \angle -68.1 + 26.79 \angle -63.02$$

$$Z = 32.23 - j73.83 \Omega$$

Determine $V_o(t)$ in the circuit.

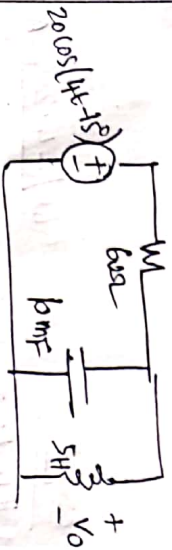


$$V_s = 20 \cos(4t - 15^\circ) = 20 \angle -15^\circ \text{ V}$$

$$\omega = 4$$

$$10 \text{ mF} = \frac{1}{j\omega C} = \frac{1}{j4 \times 10 \times 10^{-3}} = -j25 \Omega$$
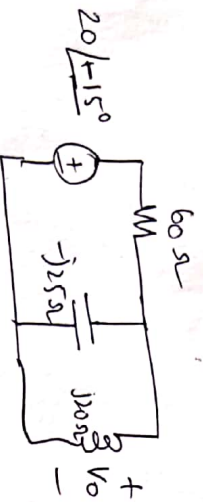
$$5 \text{ H} = j\omega L = j4 \times 5 = j20 \Omega$$




$$Z_1 = 60 \Omega \quad Z_2 = -j25 \parallel j20 = j100 \Omega$$

$$V_o = \frac{Z_2}{Z_1 + Z_2} V_s = \frac{j100}{60 + j100} (20 \angle -15^\circ)$$

$$= (0.8575 \angle 30.96^\circ) (20 \angle -15^\circ) = 17.15 \angle 15.96^\circ \text{ V}$$

$$\text{Time Domain } \Rightarrow V_o(t) = 17.15 \cos(4t + 15.96^\circ) \text{ V}$$

(2) calculate V_o

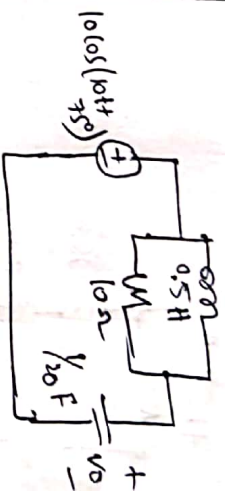

$$V_s = 10 \cos(10t - 15^\circ) \text{ V}$$

$$V_s = 10 \angle -15^\circ \text{ V}$$

$$\omega = 10 \text{ rad/sec}$$

$$Z_1 = 10 \Omega, \quad Z_2 =$$

$$Z_1 = 10 \angle -15^\circ \text{ V}$$

$$0.5 \text{ H} \Rightarrow j\omega L = j10 \times 0.5 = j5 \Omega$$

$$Z_1 = j\omega L = j10 \times 0.5 = 5 j$$

$$Z_2 = 10 \Omega$$

$$Z_3 = 1/j\omega C = 1/j10 \times 1/20 = -j2 \Omega$$

$$Z = (Z_1 \parallel Z_2) + Z_3$$

$$(5 j \parallel 10) + (-j2)$$

$$= \frac{(10 \times j5)}{(10 + j5)} - j2$$

$$= \frac{j50}{(10 + j5)} - j2$$

$$(0.5 + j10 \Omega) + (1/20 \text{ F})$$

$$2 + j4 - j2$$

$$Z_{in} = 2 + j2 \Omega$$


$$I = V/R_{in} = \frac{10 \angle 35^\circ}{2 + j2} = 3.06 + j1.76 \text{ A}$$

$$V_o = I \times Z_3 = (3.06 + j1.76 j) (-j2)$$

$$V_o(t) = 7.06 \angle -60^\circ \cos(10t - 60^\circ) \text{ V}$$

$$V_o(t) = 7.06 \cos(10t - 60^\circ) \text{ V}$$

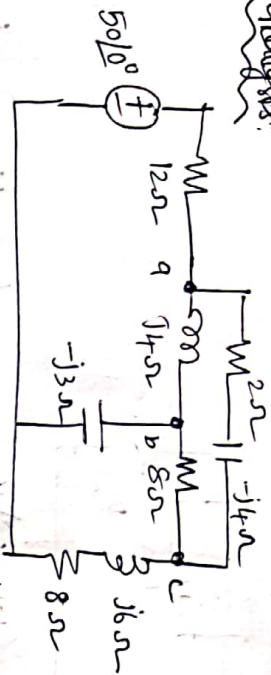Find the current I' in the circuit.
Mesh Analysis:



Delta network connected to nodes a, b, c can be converted to the Y network

$$Z_{an} = \frac{j4(2-j4)}{j4+2-j4+8} = \frac{4(4+j2)}{10} = (1.6+j0.8)\Omega$$

$$Z_{bn} = \frac{j4(8)}{j4+2-j4+8} = j3.2\Omega$$

$$Z_{cn} = \frac{8(2-j4)}{10} = (1.6-j3.2)\Omega$$

The total impedance at the source terminals is

$$Z = 12 + Z_{an} + (Z_{bn} - j3) \parallel (Z_{cn} + j6 + 8)$$


$$= 12 + 1.6 + j0.8 + (j0.2) \parallel (9.6 + j2.8)$$

$$= 13.6 + j0.8 + j0.2 \frac{(9.6 + j2.8)}{9.6 + j3}$$


$$= 13.6 + j1 = 13.64 \angle 4.204^\circ \Omega$$

The desired current is
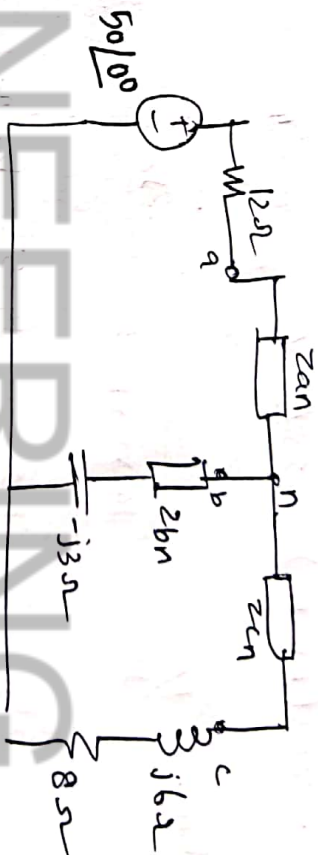
$$I = \frac{V}{Z} = \frac{50 \angle 0^\circ}{13.64 \angle 4.204^\circ} = 3.666 \angle -4.204^\circ A$$



Mesh Analysis:

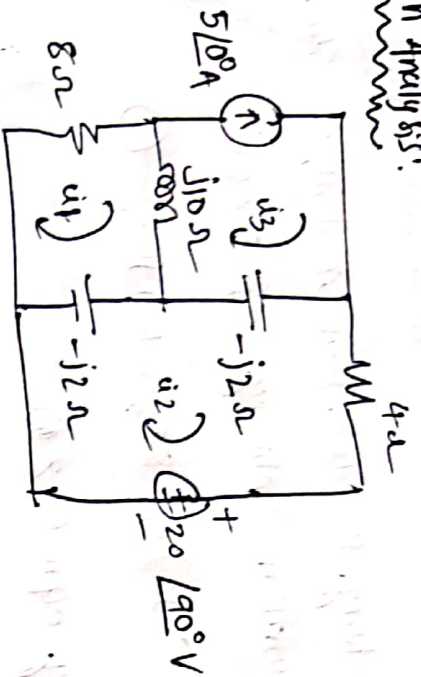

KVL @ loop 1

$$(8 + j10 - j12)I_1 - (-j12)I_2 - j10I_3 = 0 \quad \text{--- (1)}$$

KVL @ loop 2

$$(4 - j2 - j12)I_2 - (-j12)I_1 - (-j12)I_3 + 20\angle 90^\circ = 0 \quad \text{--- (2)}$$

from loop 3

$$I_3 = 5\angle 0^\circ \quad \text{--- (3) sub this in (1) & (2)}$$

$$(8 + j8)I_1 + j12I_2 = j50 \quad \text{--- (4)}$$

$$j12I_1 + (4 - j14)I_2 = -j20 - j10 \quad \text{--- (5)}$$

$$\begin{bmatrix} 8+j8 & j12 \\ j12 & 4-j14 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} j50 \\ -j30 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 8+j8 & j12 \\ j12 & 4-j14 \end{vmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} j50 \\ -j30 \end{bmatrix}$$


$$= 32(1+j)(1-j) + 4 = 68$$

$$\Delta_2 = \begin{vmatrix} 8+j8 & j50 \\ j12 & -j30 \end{vmatrix} = 340 - j240 = 416.17\angle -35.22^\circ$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{416.17\angle -35.22^\circ}{68} = 6.12\angle -35.22^\circ \text{ A}$$

$$I_0 = -I_2 = 6.12\angle 144.78^\circ \text{ A}$$

2 Solve for V_0 in the fig.

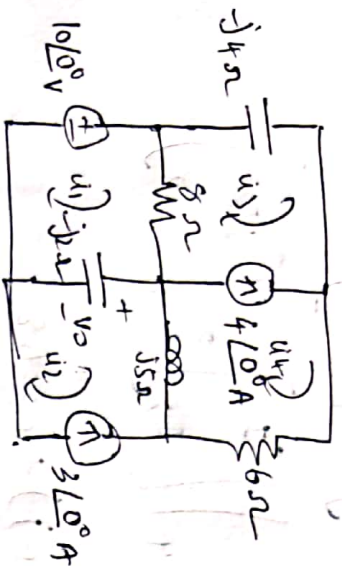

for loop 1

$$-10 + (8 - j2)I_1 - (-j2)I_2 - 8I_3 = 0$$

$$(8 - j2)I_1 + j2I_2 - 8I_3 = 10 \quad \text{--- (1)}$$

for loop 2

$$V_2 = -3 \quad \text{--- (2)}$$

for Super mesh

$$(8 - j4)I_3 - 8I_1 + (4 + j5)I_4 - j5I_2 = 0$$

From loop 3 & 4

$$I_4 = I_3 + 4 \quad \text{--- (4)}$$

Instead of solving the above four equations, we reduce them to two by elimination combining eqn 1 & 2

$$(8 - j2)I_1 - 8I_3 = 10 + j6 \quad \text{--- (5)}$$

by combining eqn 3 & 4

$$-8I_1 + (14 + j)I_3 = -24 + j35 \quad \text{--- (6)}$$

$$\Delta = \begin{vmatrix} 8 - j2 & -8 \\ -8 & 14 + j \end{vmatrix} \begin{bmatrix} I_1 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 + j6 \\ -24 + j35 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 8 - j2 & -8 \\ -8 & 14 + j \end{vmatrix} = 112 + j8 - j28 + 2 - 64 = 50 - j20$$


$$\Delta_1 = \begin{vmatrix} 10 + j6 & -8 \\ -24 + j35 & 14 + j \end{vmatrix} = 140 + j10 + j84 - 6 - 192 - j280$$

$$= -58 - j186 //$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{-58 - j186}{50 - j20} = 3.618 \angle 274.5^\circ \text{ A}$$

$$\text{Voltage } V_0 = -j2(I_1 - I_2) = -j2(3.618 \angle 274.5^\circ + 4)$$

$$= -7.2134 - j6.568 = 9.756 \angle 222.32^\circ \text{ V}$$

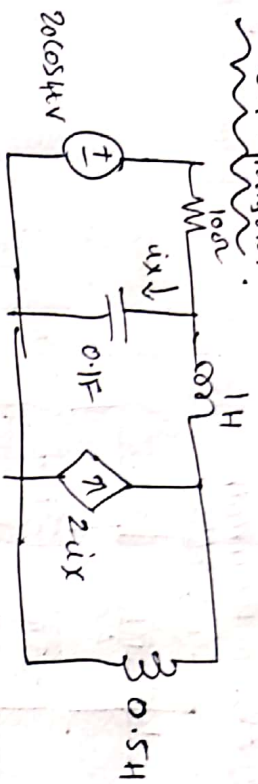Nodal Analysis:

first convert to freq. domain.


$$20\cos 4t = 20\angle 0^\circ, \quad \omega = 4 \text{ rad/s.}$$

$$1H \Rightarrow j\omega L = j4$$

$$0.5H \Rightarrow j\omega L = j2$$

$$0.1F = 1/j\omega C = -j2.5$$

freq. domain equivalent circuit.

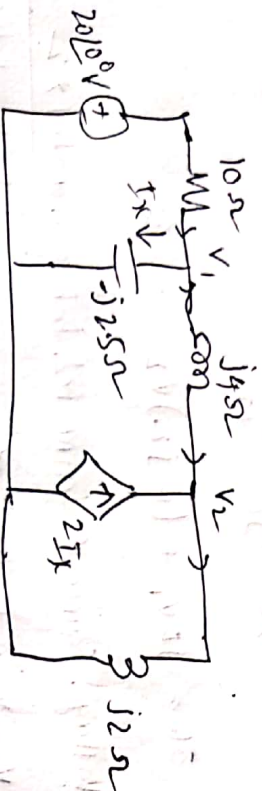

Applying KCL at node 1

$$\frac{20 - V_1}{10} = \frac{V_1}{-j2.5} + \frac{V_1 - V_2}{j4}$$

$$(1 + j1.5)V_1 + j2.5V_2 = 20 \quad \text{--- (1)}$$

At node 2

$$2I_x + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2}$$

$$\text{But } I_x = \frac{V_1}{-j2.5}$$

$$\frac{2V_1}{-j2.5} + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2}$$

Simplifying we get

$$11V_1 + 15V_2 = 0 \quad \text{--- (2)}$$

$$\begin{bmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{vmatrix} = 15 - j5$$

$$\Delta_1 = \begin{vmatrix} 20 & j2.5 \\ 0 & 15 \end{vmatrix} = 300, \quad \Delta_2 = \begin{vmatrix} 1+j1.52 & 0 \\ 11 & 0 \end{vmatrix} = -220$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{300}{15-j5} = 18.97 \angle 18.43^\circ \text{ V}$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{-220}{15-j5} = 13.91 \angle 198.3^\circ \text{ V}$$


The current I_X is given by

$$I_X = \frac{V_1}{-j2.5} = \frac{18.97 \angle 18.43^\circ}{-j2.5} = 7.59 \angle 108.4^\circ \text{ A}$$

$$= 7.59 \angle 108.4^\circ \text{ A}$$

$$i_X = 7.59 \cos(4t + 108.4^\circ) \text{ A}$$

② Compute V_1 & V_2 in the circuit.

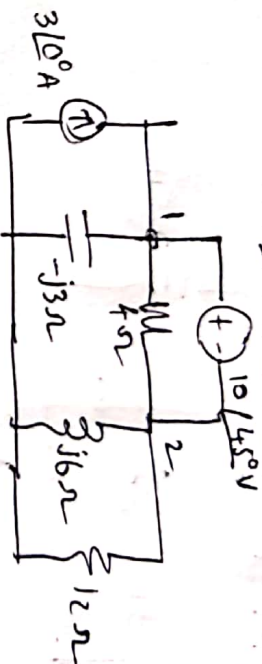

Note 1 & 2 form a supernode. $\rightarrow$ Supernode



Applying KVL

$$3 = \frac{V_1}{-j3} + \frac{V_2}{j6} + \frac{V_2}{12}$$

$$36 = j4V_1 + (1-j2)V_2 \quad \text{--- (1)}$$

But a voltage source is connected between node 1 & 2

$$\text{So } V_1 = V_2 + 10 \angle 45^\circ \quad \text{--- (2)}$$

Subs (2) in (1)

$$36 - 40 \angle 135^\circ = (1+j2)V_2 \quad \left| \quad V_2 = 31.41 \angle -87.18^\circ \text{ V} \right.$$

From (2)

$$V_1 = V_2 + 10 \angle 45^\circ = 25.78 \angle -70.44^\circ \quad \left| \quad V_1 = 25.78 \angle -70.44^\circ \text{ V} \right.$$

Instantaneous power & Average power:

Instantaneous power = instantaneous voltage $\times$ instantaneous current

$$P(t) = v(t)i(t)$$

The instantaneous power (watts) is the power at any instant of time.

Let

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

V_m & $I_m \Rightarrow$ are the amplitudes

θ_v & $\theta_i \Rightarrow$ phase angles of voltage & current respectively.

$$P(t) = v(t)i(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

$$\cos A \cos B = \frac{1}{2} [\cos(A-B) + \cos(A+B)]$$

$$P(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$

constant or time dependent

sinusoidal fn

$P(t)$ can be positive or negative

If $P(t)$ = positive $\Rightarrow$ power is absorbed by the

if $P(t)$ = negative $\Rightarrow$ Power is absorbed by the source.

Average power:

Average power in watts, is the average of the instantaneous power over one period.

$$P = \frac{1}{T} \int_0^T P(t) dt \quad \text{--- (2)}$$

Suss ② in (1)

$$P = \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) dt + \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i) dt$$

$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \frac{1}{T} \int_0^T dt + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i) \frac{1}{T} \int_0^T dt$$

$$+ \frac{1}{2} V_m I_m \frac{1}{T} \int_0^T \cos(2\omega t + \theta_v + \theta_i) dt$$

constant since it is a sine wave.

First integral is constant, second is sine wave.

Average of a sinusoid over a period is zero.

So Average power is

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

Since $\cos(\theta_v - \theta_i) = \cos(\theta_i - \theta_v) =$ difference in the phases of the voltage & current.

$P(t) =$ time varying

$P =$ does not depend on time

for instantaneous power we must know $v(t)$ & $i(t)$ (time varying)

But average power can be calculated in when the voltage & current are expressed in frequency domain or frequency domain

Eg. $V(t) = V_m \angle \theta_v$

$$I(t) = I_m \angle \theta_i$$

$$P = \frac{1}{2} V I = \frac{1}{2} V_m I_m \angle \theta_v - \theta_i$$

$$= \frac{1}{2} V_m I_m [\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i)]$$

Real part of this equation is average power.

$$P = \frac{1}{2} \operatorname{Re}[VI^*]$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

when $\theta_v = \theta_i$

$$P = \frac{1}{2} V_m I_m = \frac{1}{2} I_m^2 R = \frac{1}{2} |I|^2 R$$

when $\theta_v - \theta_i = 90^\circ$
(Shows the circuit is Purely reactive)

$$P = \frac{1}{2} V_m I_m \cos 90^\circ = 0$$

Shows that the circuit is purely reactive.
Circuit absorbs no average power

A resistive load (R) absorbs power at all times,
while a reactive load (L or C) absorbs zero
average power

① Problem

Given that

$$v(t) = 120 \cos(377t + 45^\circ) \text{ V}$$

$$i(t) = 10 \cos(377t - 10^\circ) \text{ A}$$

Find the instantaneous power & average power
absorbed by the passive linear NTK.

Instantaneous power

$$P = v i = 1200 \cos(377t + 45^\circ) \cos(377t - 10^\circ)$$

$$P(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$

$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$

$$= 600 [\cos(754t + 35^\circ) + \cos(754t + 55^\circ)]$$

$$P(t) = 344.2 + 600 \cos(754t + 35^\circ) \text{ W}$$

Average power P_{avg}

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} (1200) 10 \cos(45^\circ - (-10^\circ))$$

$$= 600 \cos 55^\circ = \underline{\underline{344.2 \text{ W}}}$$

- ② Calculate the instantaneous power & average power absorbed by the passive linear NT.

$$v(t) = 80 \cos(10t + 20^\circ) \text{ V}$$

$$i(t) = 15 \sin(10t + 60^\circ) \text{ A}$$

$i(t)$ can be written as

$$i(t) = 15 \cos(10t + 60^\circ - 90^\circ) \text{ A}$$

$$i(t) = 15 \cos(10t - 30^\circ) \text{ A}$$

$$p(t) = \frac{1}{2} v_m i_m \cos(\theta_v - \theta_i) + \frac{1}{2} v_m i_m \cos(2\omega t + \theta_v + \theta_i)$$

$$= \frac{1}{2} 80 \times 15 \cos(20 - (-30)) + \frac{1}{2} 80 \times 15 \cos(2 \times 10t + 20 - 30)$$

$$= 600 \cos(50^\circ) + \frac{1}{2} 600 \cos(20t - 10^\circ)$$

$$P(t) = 385.7 + 600 \cos(20t - 10^\circ) \text{ W}$$

Average Power P_{avg}

$$P_{avg} = \frac{1}{2} v_m i_m \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} \times 80 \times 15 \cos(20 - (-30))$$

$$= 600 \cos(50^\circ)$$

$$P_{avg} = 385.7 \text{ W}$$

- ③ Calculate the average power absorbed by an impedance $Z = 30 - j70 \Omega$ when a voltage $V = 120 \angle 0^\circ$ is applied across it.

$$I = \frac{V}{Z} = \frac{120 \angle 0^\circ}{30 - j70} = \frac{120 \angle 0^\circ}{76.16 \angle -66.8^\circ} = 1.596 \angle 66.8^\circ \text{ A}$$

$$P_{avg} = \frac{1}{2} v_m i_m \cos(\theta_v - \theta_i) = \frac{1}{2} (120)(1.596) \cos(0 - 66.8^\circ)$$

$$P_{avg} = 33.24 \text{ W}$$

- (4) A current $I = 10 \angle 30^\circ$ flows through an impedance $Z = 20 \angle -22^\circ \Omega$, Find the average power delivered to the impedance.

$$V = I \cdot Z = 10 \angle 30^\circ \times 20 \angle -22^\circ$$

$$V = 198.05 \angle 8^\circ \text{ V}$$

$$\begin{aligned} P_{\text{avg}} &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \\ &= \frac{1}{2} \times 200 \times 10 \cos(8^\circ - 30^\circ) \\ &= 1000 \cos(-22^\circ) \end{aligned}$$

$$P_{\text{avg}} = 927.2 \text{ W}$$

- (5) Find the avg. power supplied by the source & the avg power ~~absorbed~~ absorbed by the resistor



$$I = \frac{5 \angle 30^\circ}{4 - j2} = \frac{5 \angle 30^\circ}{4.472 \angle -26.57^\circ} = 1.118 \angle 56.57^\circ \text{ A}$$

$$P_{\text{avg}} = \frac{1}{2} (5) (1.118) \cos(30^\circ - 56.57^\circ) = 2.5 \text{ W}$$

Current through resistor is

$$I_R = I = 1.118 \angle 56.57^\circ \text{ A}$$


$$V_R = 4 I_R = 4.472 \angle 56.57^\circ \text{ V}$$

Power absorbed by resistor is

$$P = \frac{1}{2} (4.472) (1.118) = 2.5 \text{ W}$$

(Since phase diff bet voltage & current is zero)
($\theta_v - \theta_i = 0$)

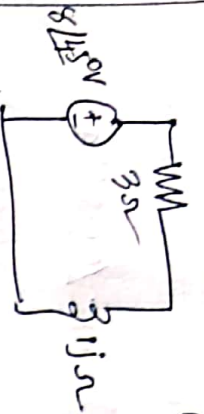which is the same as the average power delivered by the zero average power is absorbed by the capacitor.



Calculate the Power (avg) absorbed by the resistor & inductor. Find the avg power supplied by voltage source.

$$I = \frac{8\angle 45^\circ \text{ V}}{3 + j1} = \frac{8\angle 45^\circ}{3.16\angle 18.43^\circ} = 2.53\angle 26.57^\circ \text{ A}$$

Power by supply ..

$$P_{\text{avg}} = \frac{1}{2} \times 8 \times 2.53 \cos(45^\circ - 26.57^\circ)$$

$$P_{\text{avg (supply)}} = 9.6 \text{ W}$$

Current through Resistor

$$I = \frac{8\angle 45^\circ}{3} = 2.66\angle 45^\circ \text{ A}$$

$$P_{\text{avg (res)}} = \frac{1}{2} \times 8 \times 2.66 \cos(45^\circ - 45^\circ)$$

Current through resistor. $I = 2.53\angle 26.57^\circ \text{ A}$

$$\text{Voltage in resistor } (2.53\angle 26.57^\circ \times 3) = 7.59\angle 26.57^\circ$$

$$P_{\text{loss in resistor}} = \frac{1}{2} \times 8 \times 2.53 \times 2.53 \cos(26.57 - 26.57) = \frac{1}{2} \times 8 \times 2.53 \times 2.53$$


$$P_{\text{avg res.}} = 9.6 \text{ W}$$

absorbed by

Power in Inductor is zero.

③ Determine the average power generated by each source

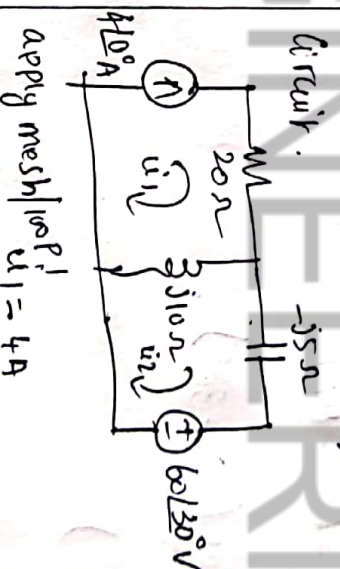and the power absorbed by each passive elements of the circuit.



$$\text{apply mesh loop } i_1 = 4 \text{ A}$$

From mesh/loop 2

$$(j10 - j5)I_2 - j10I_1 + 60\angle 30^\circ = 0$$

$$j5I_2 = -60\angle 30^\circ + j40 \Rightarrow I_2 = -12\angle -60^\circ + 8 = 10.58\angle 79.1^\circ \text{ A}$$

For the voltage source, the current flowing from it is I_2

$$I_2 = 10.58 \angle 39.1^\circ \text{ A}$$

A voltage is $60 \angle 30^\circ \text{ V}$ so avg. power is

$$P_s = \frac{1}{2} (60)(10.58) \cos(30^\circ - 39.1^\circ) = \underline{\underline{207.8 \text{ W}}}$$

Thus avg. power is absorbed by the source, in view of the direction of I_2 & polarity of the voltage source the Ctr is delivering average power to the voltage source.

for the current source: $I_1 = 4 \angle 0^\circ$.

$$\begin{aligned} V_1 &= 20 I_1 + j10 (I_1 - I_2) = 80 + j10(4 - 2 - j10.39) \\ &= 183.9 + j20. \\ &= 184.984 \angle 6.21^\circ \text{ V} \end{aligned}$$

The avg. power supplied by the current source is

$$P_1 = \frac{1}{2} (184.984)(4) \cos(6.21^\circ - 0^\circ) = \underline{\underline{-367.8 \text{ W}}}$$

Negative sign indicates the current source is supplying power to the circuit.

For the resistor the current through it is $I_1 = 4 \angle 0^\circ$

Voltage across it is $20 I_1 = 80 \angle 0^\circ$;

$$P_2 = \frac{1}{2} (80)(4) = \underline{\underline{160 \text{ W}}}$$

For the capacitor, the current through it is $I_2 = 10.58 \angle 39.1^\circ$

$$\begin{aligned} \text{& the voltage across it is } -j5 I_2 &= (5 \angle -90^\circ)(10.58 \angle 39.1^\circ) \\ &= 52.9 \angle -39.1^\circ - 90^\circ. \end{aligned}$$

avg. power absorbed by capacitor is

$$P_3 = \frac{1}{2} (52.9)(10.58) \cos(-90^\circ) = 0$$

Inductor, current is $(I_1 - I_2) = 2 - j10.39 = 10.58 \angle -39.1^\circ$

Voltage across i_1 is $110(I_1 - I_2) = 10.58 \angle -99.1 + 90^\circ$

Hence the average power absorbed by the inductor is

$$P_3 = \frac{1}{2} (10.58)(10.58) \cos 90^\circ = 0$$

Notice that the inductor & the capacitor absorb zero average power and that the total power supplied by

the current source equals the power absorbed by the resistor & the voltage source or

$$P_1 + P_2 + P_3 + P_4 + P_5 = -36 - 8 + 100 + 0 + 0 = 209.6 \approx 0$$

indicating that power is conserved.

Effective or rms value:

The effective value of a periodic current is the dc current that delivers the same average power to a resistor as the periodic current.

$$I_{\text{eff}} = I_{\text{rms}}$$

$$V_{\text{eff}} = V_{\text{rms}}$$

TELEGRAM: @eduengineering

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2}}$$

Average power can be written in terms of rms values

$$P = I_{\text{rms}}^2 R = \frac{V_{\text{rms}}^2}{R}$$

Apparent power & Power factor:-

Apparent power (in VA) is the product of the rms values of voltage and current.

(units (volt-amp))

Power factor:- Ratio of average power to apparent power

$$P_f = \frac{P}{S} = \cos(\theta_v - \theta_i)$$

$\theta_v - \theta_i$ = Power factor angle.

Power factor is the cosine of the phase difference between voltage & current. It is also the cosine of the angle of load

① A Series-connected load draws a current $i(t) = 4 \cos(400\pi t + 10^\circ) \text{ A}$ when the applied voltage is $v(t) = 120 \cos(100\pi t - 20^\circ) \text{ V}$, find the Apparent Power & the Power factor of the load, determine the element values that form the Series-connected load.

$$\text{Apparent Power } S = V_{\text{rms}} I_{\text{rms}} = \frac{120}{\sqrt{2}} \times \frac{4}{\sqrt{2}} = \underline{\underline{240 \text{ VA}}}$$

$$\text{Power factor } P_f = \cos(\theta_v - \theta_i) =$$

$$= \cos(-20 - 10) = 0.866 \text{ (leading)} \\ \text{(Because current leads voltage)}$$

$$Z = \frac{V}{I} = \frac{120 \angle -20^\circ}{4 \angle 10^\circ} = 25.98 - j15 \Omega$$

$$P_f = \cos(-30^\circ) = 0.866 \text{ (leading)}$$

Load impedance Z can be modeled by a

25.98Ω resistor in series with a capacitor

$$X_C = -15 = -1/\omega C$$

$$C = 1/15\omega = 1/15 \times 1000 = 2122 \mu\text{F}$$

② Obtain Power factor & the Apparent Power of a load whose impedance is $Z = 60 + j40 \Omega$ $v(t) = 150 \cos(377t + 10^\circ) \text{ V}$

Apparent Power $S = V_{\text{rms}} I_{\text{rms}}$:

$$I(t) = \frac{v(t)}{Z} = \frac{150 \angle 10^\circ}{60 + j40} = \frac{150 \angle 10^\circ}{72.11 \angle 33.69^\circ}$$

$$I(t) = \underline{\underline{2.08 \angle -23.69^\circ \text{ A}}}$$

$$S = V_{\text{rms}} I_{\text{rms}} = \frac{150}{\sqrt{2}} \times \frac{2.08}{\sqrt{2}} = \underline{\underline{156 \text{ VA}}}$$

$$P_f = \cos(\theta_v - \theta_i) =$$

$$= \cos(10 + 23.69) = 0.832 \text{ (lagging)}$$

(Because current lags voltage)

Complex Power: $\text{in}(VA)$

is the product of the rms voltage phasor and the complex conjugate of the rms current phasor. Also complex quantity in real part is real power P & in imaginary part is reactive power Q .

$$\begin{aligned}\text{Complex power} = S &= P + jQ = \frac{1}{2} V I^* \\ &= V_{\text{rms}} I_{\text{rms}} \angle \theta_V - \theta_I\end{aligned}$$

$$\text{Apparent Power } S = |S| = V_{\text{rms}} I_{\text{rms}} = \sqrt{P^2 + Q^2}$$

$$\text{Real Power } P = \text{Re}(S) = S \cos(\theta_V - \theta_I)$$

$$\text{Reactive Power } Q = \text{Im}(S) = S \sin(\theta_V - \theta_I)$$

$$\text{Power factor} = \frac{P}{S} = \cos(\theta_V - \theta_I)$$

Problem:

- ① The voltage across a load is $v(t) = 60 \cos(\omega t - 10^\circ) V$ and the current through the element in the direction of the voltage drop is $i(t) = 1.5 \cos(\omega t + 50^\circ) A$.
- Find (a) complex & apparent powers

(b) real & reactive power

(c) power factor & the load impedance.

②

$$V_{\text{rms}} = \frac{60}{\sqrt{2}} \angle -10^\circ \quad I_{\text{rms}} = \frac{1.5}{\sqrt{2}} \angle 50^\circ$$

$$\text{Complex Power} = V_{\text{rms}} I_{\text{rms}}^* = \left(\frac{60}{\sqrt{2}} \angle -10^\circ \right) \left(\frac{1.5}{\sqrt{2}} \angle -50^\circ \right)$$

$$\text{Complex Power} = 45 \angle -60^\circ VA$$

Apparent Power

$$S = |S| = 45 VA$$

⑥ we can express the complex power in rectangular form

$$S = 45 \angle -60^\circ = 45 [\cos(-60) + j \sin(-60^\circ)] \\ = 22.5 - j38.97$$

Since $S = P + jQ$, the real power is

$$\text{Real power } P = 22.5 \text{ W}$$

while reactive power is

$$Q = -38.97 \text{ VAR}$$

⑦ The power factor

$$P_f = \cos(-60^\circ) = 0.5 \text{ (leading)}$$

$$Z = \frac{V}{I} = \frac{60 \angle -10^\circ}{1.5 \angle +50^\circ} = 40 \angle -60^\circ \Omega$$

⑬

② for a load $V_{rms} = 110 \angle 85^\circ \text{ V}$, $I_{rms} = 0.4 \angle 15^\circ \text{ A}$

Determine complex power, apparent power, real power, reactive power, power factor & load impedance.

Complex power

$$S = V_{rms} I_{rms}^*$$

$$S = \frac{110}{\cancel{100}} \angle 85^\circ \times 0.4 \angle 15^\circ$$

$$S = 44 \angle 70^\circ \text{ VA}$$

Apparent power:

$$|S| = 44 \text{ VA}$$

Real power

Complex power in rectangular form

$$15.04 + j41.3 \text{ W}$$

$$S = P + jQ$$

Real Power $P = 15.04 \text{ W}$

Reactive Power $Q = 41.3 \text{ VAR}$

Power factor

$$PF = \cos(\theta_v - \theta_i) \quad \text{or} \quad PF = \cos(\theta)$$

$$= \cos(85^\circ - 15^\circ)$$

$$= \cos(70^\circ)$$

from complex power

$$PF = 0.342 \text{ lagging}$$

Impedance

$$Z = \frac{V}{I} = \frac{V_{\text{rms}} \angle \theta_v}{I_{\text{rms}} \angle \theta_i} = \frac{110 \angle 85^\circ}{0.4 \angle 15^\circ}$$

$$= 275 \angle 70^\circ \Omega$$

$$Z = 94.05 + j258.4 \Omega$$

⑤

For a load $V_{\text{rms}} = 110 \angle 85^\circ \text{ V}$, $I_{\text{rms}} = 0.4$

③

A load Z draws 12 kVA at a P.F. of 0.856

lagging from a 120 V rms sinusoidal source. Calculate

the average & reactive power delivered to the load,

(b) Peak current and the (c) load impedance.

Given that $PF = \cos \theta = 0.856$, we obtain the

$$\text{Power angle } \theta = \cos^{-1} 0.856 = 31.13^\circ$$

If apparent power is $S = 12000 \text{ VA}$ the average

or real power is

$$P = S \cos \theta = 12000 \times 0.856 = 10.272 \text{ kW}$$

where the Reactive power is

$$Q = S \sin \theta = 12000 \times 0.517 = 6204 \text{ kVAR}$$

(v) Since the PF is lagging, the complex power is

$$S = P + jQ = 10.272 + j6.204 \text{ kVA}$$

$$\text{From } S = V_{\text{rms}} I_{\text{rms}}^*$$

$$I_{\text{rms}}^* = \frac{S}{V_{\text{rms}}} = \frac{10,272 + j6204}{120 \angle 0^\circ}$$

$$= 85.6 + j51.7 \text{ A}$$

$$= \underline{\underline{100 \angle 31.13^\circ \text{ A}}}$$

Thus $I_{\text{rms}} = 100 \angle -31.13^\circ$ & the peak current is

$$I_{\text{m}} = \sqrt{2} I_{\text{rms}} = \sqrt{2} \times 100 = \underline{\underline{141.4 \text{ A}}}$$

The load impedance

$$Z = \frac{V_{\text{rms}}}{I_{\text{rms}}} = \frac{120 \angle 0^\circ}{100 \angle -31.13^\circ} = \underline{\underline{1.2 \angle 31.13^\circ \Omega}}$$

which is an inductive impedance.



EDU ***ENGINEERING***

PIONEER OF ENGINEERING NOTES

CONNECT WITH US



WEBSITE: www.eduengineering.in



TELEGRAM: [@eduengineering](https://t.me/eduengineering)

- Best website for **Anna University Affiliated College** Students
- Regular Updates for all Semesters
- All **Department Notes** AVAILABLE
- All **Lab Manuals** AVAILABLE
- **Handwritten** Notes AVAILABLE
- **Printed** Notes AVAILABLE
- **Past Year** Question Papers AVAILABLE
- Subject wise **Question Banks** AVAILABLE
- Important Questions for Semesters AVAILABLE
- Various Author Books AVAILABLE

