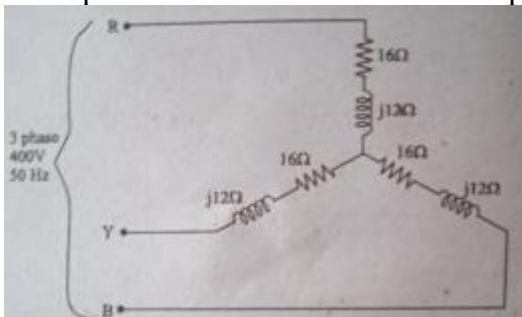
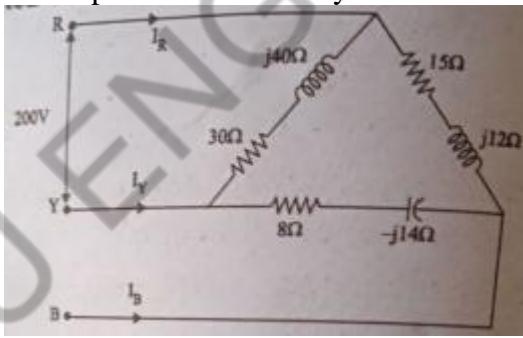


UPC QUESTIONS

Unit 5 Three phase circuits

S.No	Question	Grade	Grade	Mark
1	<p>1. An balanced star connected four wire load has a balanced supply voltage of 400 V. The load impedance are $Z_R = (16 + j12)$, $Z_Y = (16 + j12)$, $Z_B = (16 + j12)$. Calculate the line current, neutral currents and total power? And also draw the phasor diagram of the same.</p> 	A		
2	<p>An unbalanced delta connected load has a supply voltage of 200 V. The load impedance are given in figure below. Calculate the line currents, phase currents and total power consumed by the load?</p> 	B		
3	<p>Calculate the total power input and readings of the two wattmeter connected to measure power in a three phase balanced load, if the reactive power input is 15 KVAR and the load power factor is 0.8. Also compute load KVA?</p>	A		
4	<p>Derivation of Power measurement by 2 wattmeter method?</p>	A		
5	<p>Calculate the reading of the two wattmeters (W1 and W2) connected to measure the total power for a balanced star connected load shown in figure below fed from a three phase 400 V balanced supply with phase sequence as RYB. The load impedance per phase is $20 + j15$. Also find the line and phase currents, power factor, total power, total reactive VA and total VA?</p>	A		

6	An unbalanced star connected four wire load has a balanced supply voltage of 400 V. The load impedance are $Z_R = (4 + j8)$ ohm , $Z_Y = (3 + j4)$, $Z_B = (15 + j10)$. Calculate the line current, neutral currents and total power? And also draw the phasor diagram of the same.	A	
7	Find the currents I_a , I_b and I_c for the given circuits 	A	
8	Show that (i) in a star connected network, line voltage= $\sqrt{3}$ times phase voltage, and (ii) in delta connected network line current= $\sqrt{3}$ times phase current?	A	
9	The input power to a 3 phase load is 10 KW at 0.9 pf. The wattmeter's are connected to measure power, Find the individual readings of the wattmeter?	A	
10	A Three phase, balanced delta connected load of $(4+j8)$ ohm is connected across a 400 v, 3 phase balanced supply. Determine the phase currents and line currents?		B